

Physics 375, Laboratory 6  
Transistor Properties

### Overview

The purpose of this experiments is to measure the current-voltage curves of different types of transistors and to use them in simple DC circuits.

### Background

The zener diode is a diode designed to run with reverse bias. When the reverse current exceeds a specified minimum, the voltage drop across the zener becomes constant independent of the reverse current.


The transistor is a non-ohmic device with three-terminals. There are two basic types of transistors, the field effect transistor (FET) and the bipolar junction transistor (BJT).

A junction field effect transistor (JFET) is made from a junction of a p-type and n-type semiconductor, but the junction is used to control the conductance in one of the semiconductor layers. The drain and source terminals are connected to ends of one semiconductor, and the gate is connected to the other semiconductor. The transconductance  $g_m$  measures the ratio of the out put current to the applied voltage.


A bipolar junction transistor (BJT) is made from two junctions of a p-type and n-type semiconductor. The base-emitter junction acts like a diode. However, when a current flows from the base to emitter ( $I_B$ ) of the transistor, a current is induced to flow from the collector to emitter ( $I_C$ ) such that  $I_C = \beta I_B$ , where  $\beta$  is a characteristic factor for the transistor.
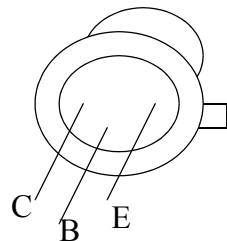
### Components

The 2N2222 is a general purpose npn transistor. The 2N2222 comes in a TO-18 metal case with leads for emitter, base and collector.



2N2222

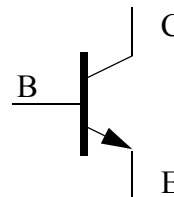


The 2N2222 has maximum ratings as follows:

$$V_{CE} < 40 \text{ V}, V_{CB} < 60 \text{ V}, V_{EB} < 6.0 \text{ V}$$

$$I_C < 800 \text{ mA}, P = I_C V_{CE} < 1 \text{ W}, \beta \text{ is between } 50 \text{ and } 200$$

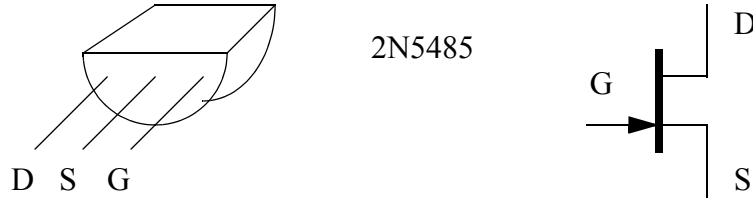The 2N5485 is an n-channel JFET and comes in a TO-92 plastic case with leads for drain, source and gate.



The 2N5485 has maximum ratings as follows:

$$V_{DG} < 25 \text{ V}, -V_{GS} < 25 \text{ V}$$

$$I_D < 30 \text{ mA}, P = I_D V_{DS} < 300 \text{ mW}$$

### 1. DC JFET Curves

Connect two power supplies an n-channel transistor (2N5485), potentiometer, and resistor as in figure 1.

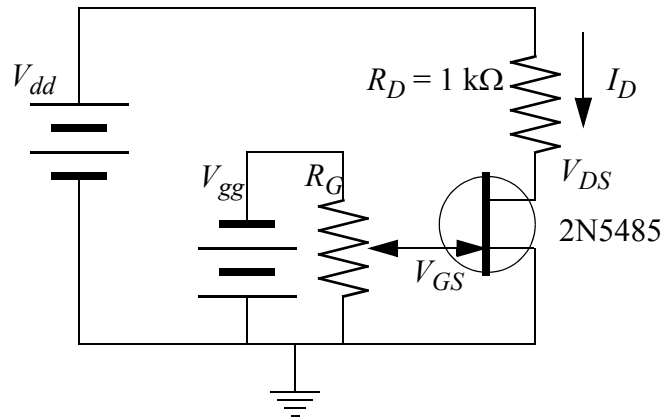


Figure 1: DC JFET Measurement

Use the fixed -15 V power supply for  $V_{gg}$  (note the inverted polarity on the schematic) and a 10 kΩ potentiometer as  $R_G$  to set the voltage at the gate  $V_{GS}$ . Use the variable power supply for  $V_{dd}$ . Set  $V_{GS} = 0 \text{ V}$  and  $V_{dd} = 0.5 \text{ V}$ , and measure  $V_{DS}$  with a DMM. Subtract  $V_{DS}$  from  $V_{dd}$  to get the voltage drop across  $R_D$ , and use that to calculate  $I_D$ . Repeat the measurement of  $V_{DS}$  and  $I_D$  for  $V_{dd} = 1.0, 2.0, 4.0, 6.0, 10.0,$  and  $15.0 \text{ V}$ , and graph  $I_D$  vs.  $V_{DS}$ . Find the curve of  $I_D$  vs.  $V_{DS}$  again for  $V_{GS} = -0.5 \text{ V}$ , and  $-1.0 \text{ V}$ . Plot the three curves on a single graph. Plot  $I_D$  vs.  $V_{DS}$  for the region of constant  $I_D$ . Calculate  $g_m = \Delta I_D / \Delta V_{GS}$ .

## 2. BJT Transistor Curves

Connect the variable power supply, an npn transistor (2N2222), resistor, and DMM:

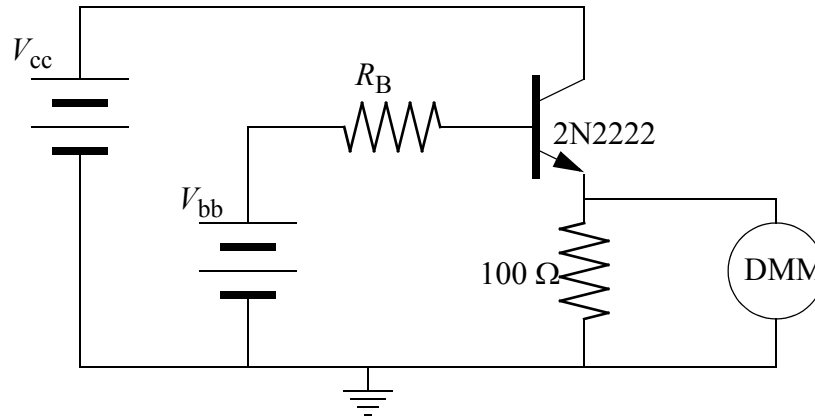


Figure 2: DC BJT Measurement

Use a 1.5 V battery for  $V_{bb}$  and the variable power supply for  $V_{cc}$ . Use  $R_B = 470 \text{ k}\Omega$ , and  $V_{cc} = 0.1 \text{ V}$ , and measure the voltage drop across  $R_B$  to get  $I_B$ . Now measure the voltage across the 100  $\Omega$  resistor,  $V_E$ . Calculate  $V_{CE}$  and  $I_C$  at this value of  $I_B$ . Repeat the measurement of  $V_E$  for  $V_{cc} = 0.2, 0.5, 1, 2, \text{ and } 5 \text{ V}$ , and graph  $I_C$  vs.  $V_{CE}$ . Change  $R_B = 220 \text{ k}\Omega$  and repeat the measurement of the curve. Find a third curve by using  $R_B = 100 \text{ k}\Omega$ . What value can be derived for  $\beta$  for this transistor.

### 3. Voltage Source

Build the following circuit using a variable power supply for  $V_{CC}$  and the DMM to measure  $V_{out}$ .

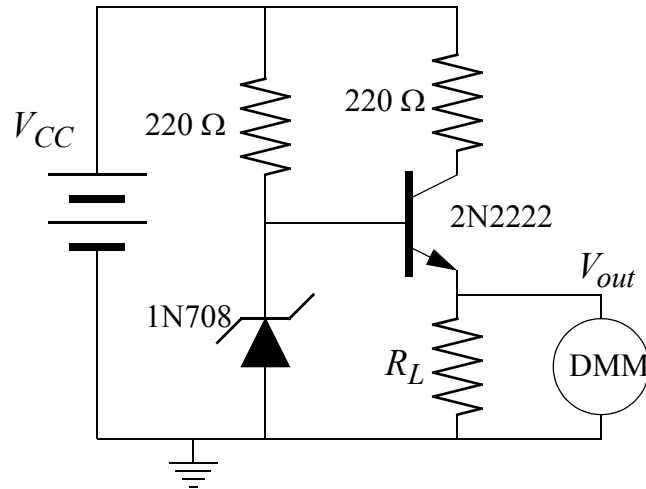


Figure 2: Transistor Voltage Source

Set  $V_{CC} = 12$  V and use  $R_L = 100$  k $\Omega$ . Measure  $V_{out}$ . Reduce  $V_{CC}$  in 2 V steps and measure  $V_{out}$  for each step. Set  $V_{CC} = 12$  V and remove  $R_L$  and measure  $V_{out} = V_{th}$  the Thevenin equivalent voltage for the circuit. Put in  $R_L = 1$  k $\Omega$  and measure  $V_{out}$ . The Thevenin equivalent resistance for the voltage source forms a voltage divider with  $R_L$ . Use the measurement of  $V_{out}$  with a load compared to  $V_{th}$  to calculate the Thevenin resistance for the voltage source.