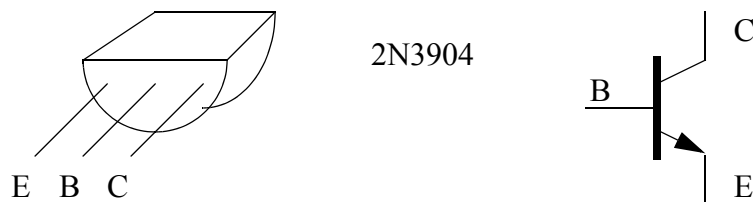


### Overview

The purpose of these experiments is to measure AC signal amplification, input and output impedance using a common-emitter amplifier and a source-follower amplifier.

### Background

The 2N3904 is a general purpose npn transistor. The 2N3904 comes in a TO-92 plastic case with leads for emitter, base and collector.



The 2N3904 has maximum ratings as follows:

$$V_{CE} < 40 \text{ V}$$


$$V_{CB} < 60 \text{ V}$$

$$V_{EB} < 6.0 \text{ V}$$

$$I_C < 200 \text{ mA}$$

$$P = I_C V_{CE} < 625 \text{ mW}$$

A junction field effect transistor (JFET) is made from a junction of a p-type and n-type semiconductor, but the junction is used to control the conductance in one of the semiconductor layers. In many ways a JFET behaves like a bipolar junction transistor with the drain, source and gate equivalent to the collector, emitter and base. The 2N5485 is an n-channel JFET and comes in a TO-92 plastic case with leads for drain, source and gate.

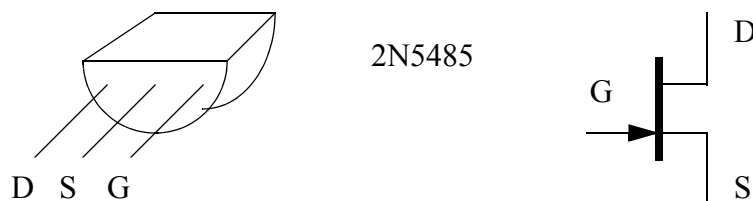

The 2N5485 has maximum ratings as follows:

$$V_{DG} < 25 \text{ V}, -V_{GS} < 25 \text{ V}$$

$$I_D < 30 \text{ mA}, P = I_D V_{DS} < 300 \text{ mW}$$

## 1. Signal Amplifier

Build the circuit in figure 1 using a 2N3904 transistor.

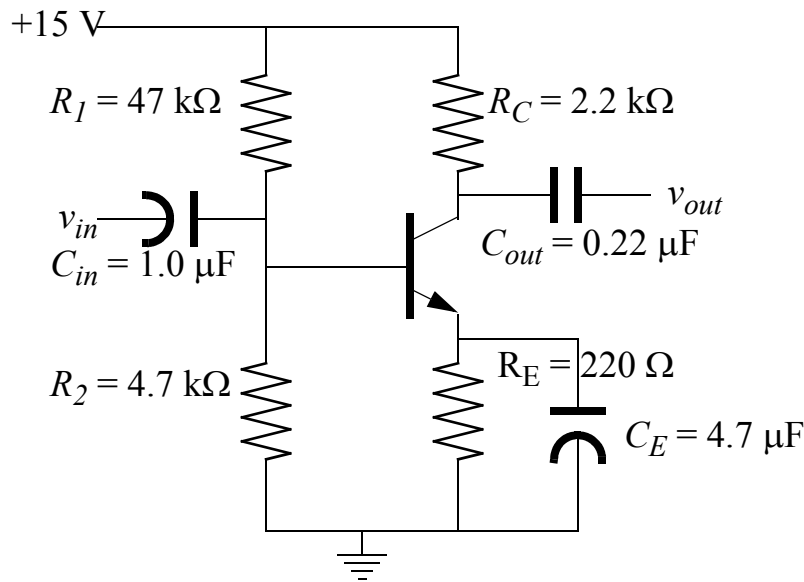


Figure 1: Common Emitter Amplifier

Build the circuit and measure  $V_B$ ,  $V_C$  and  $V_E$  and compare to the expected values for DC operation. Use a sine wave generator (no DC offset) for  $v_{in}$  and an oscilloscope to measure both  $v_{in}$  and  $v_{out}$ . Measure the gain  $A$  vs. frequency  $f$  for  $f = 50$  Hz, 100 Hz, 200 Hz, 500 Hz, 1 kHz, 2 kHz, 5 kHz, 10 kHz, 20 kHz and 100 kHz. Compare the gain to the expected value

$$A = \frac{-\beta R_C}{h_{ie} + Z_E} \quad Z_E = \frac{Z_{R_E} Z_{C_E}}{Z_{R_E} + Z_{C_E}}$$

Remove the emitter bypass capacitor  $C_E$  and measure gain vs. frequency again.

## 2. Amplifier Impedance

Measure the impedance of the amplifier of figure 1 by creating a voltage divider and measuring the change in signal. To measure the input impedance, place a known resistor  $R_S$  in series before the input capacitor and operate the function generator at 1 kHz. The gain in the signal will change according to the following formula:

$$A' = \frac{Z_{in}}{R_S + Z_{in}} A \quad Z_{in} = \frac{1}{A/A' - 1} R_S$$

Try different resistors to get a good measure of the gain. The best result will occur when  $R_S$  is about equal to  $Z_{in}$  so that  $A/A'$  is about 2. To measure the output impedance place a known resistor  $R_L$  from the output to ground to form a voltage divider. The gain in the signal will change:

$$A' = \frac{R_L}{R_L + Z_{out}} A \quad Z_{out} = (A/A' - 1)R_S$$

The input impedance should be roughly the parallel impedance of the base bias resistors and  $h_{ie}$ . The output impedance should be roughly the parallel impedance of the collector resistor and  $50h_{ie}$ . How well does your circuit compare to the expected impedance?

### 3. FET Follower

Build the circuit in figure 2 using a 2N5485 transistor.

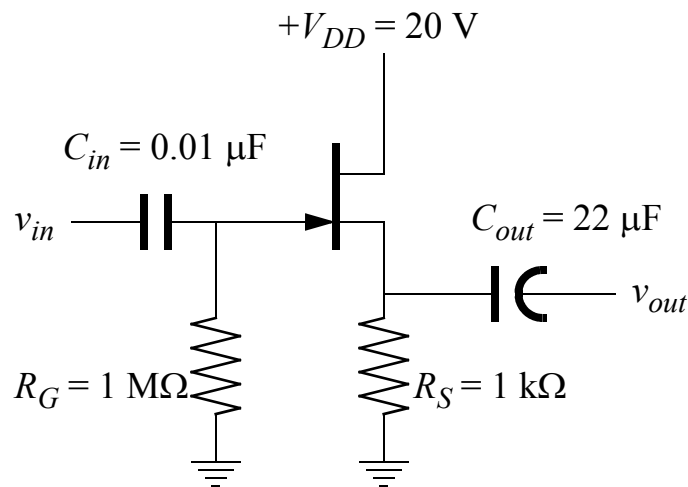


Figure 2: Source Follower Amplifier

Measure  $V_G$  and  $V_S$ , calculate  $I_D$  and compare to the expected values for DC operation. Use a sine wave generator (no DC offset) for  $v_{in}$  and an oscilloscope to measure both  $v_{in}$  and  $v_{out}$ . Measure the gain  $A$  vs. frequency  $f$  for  $f = 50$  Hz, 100 Hz, 200 Hz, 500 Hz, 1 kHz, 2 kHz, 5 kHz, 10 kHz, 20 kHz and 100 kHz. Measure the input and output impedance of the circuit using the method of part 2.