

Kirchhoff's Laws



1. Kirchhoff Current Law

The sum of currents entering a junction is equal to the sum of currents leaving the junction.

2. Kirchhoff Voltage Law

The sum of voltage increases around a closed loop of a circuit is equal to the sum of voltage drops around the loop.

- **Branch Method**

Label a current through each branch of the circuit.

Set up a set of independent equations for the junctions (current law) and loops (voltage law) in the circuit.

- **Loop Current Method**


Label a current around each independent loop of the circuit.

Set up an equation for each current loop (voltage law), counting all the currents in any given element.

- **Nodal Method**

Like loop current, but an unknown voltage is assigned to each junction. Currents found from Ohm's Law

Branch Example

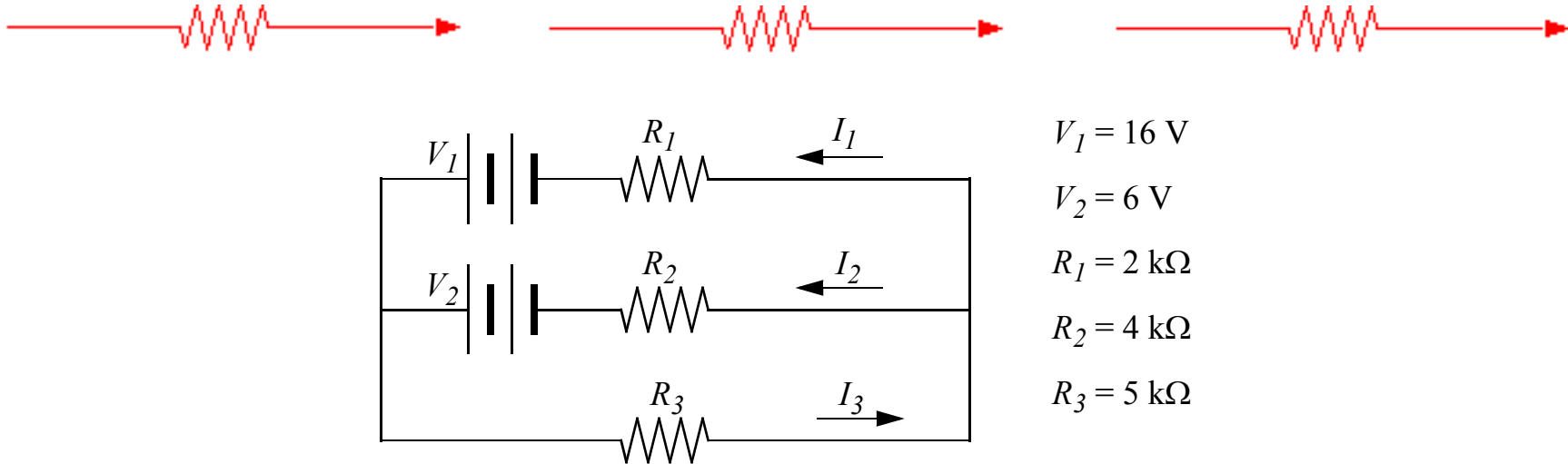

$$V_1 = 16 \text{ V}$$

$$V_2 = 6 \text{ V}$$

$$R_1 = 2 \text{ k}\Omega$$

$$R_2 = 4 \text{ k}\Omega$$

$$R_3 = 5 \text{ k}\Omega$$

- Current law: $I_3 = I_1 + I_2$
- Voltage law: $V_1 - V_2 = R_1 I_1 - R_2 I_2$ and $V_2 = R_2 I_2 + R_3 I_3$
- Solve for I_1 , substituting for I_3 and I_2 :

$$V_2 = R_2 I_2 + R_3 I_1 + R_3 I_2$$

$$V_2 = R_1 I_1 + V_2 - V_1 + R_3 I_1 + (R_3 / R_2)(R_1 I_1 + V_2 - V_1)$$

$$R_1 R_2 I_1 + R_2 R_3 I_1 + R_1 R_3 I_1 = R_2 V_1 + R_3 V_1 - R_3 V_2$$

$$I_1 = (R_2 V_1 + R_3 V_1 - R_3 V_2) / (R_1 R_2 + R_2 R_3 + R_1 R_3)$$


- Finally,

$$I_1 = 3 \text{ mA}, I_2 = -1 \text{ mA}, I_3 = 2 \text{ mA}.$$

Series Resistors



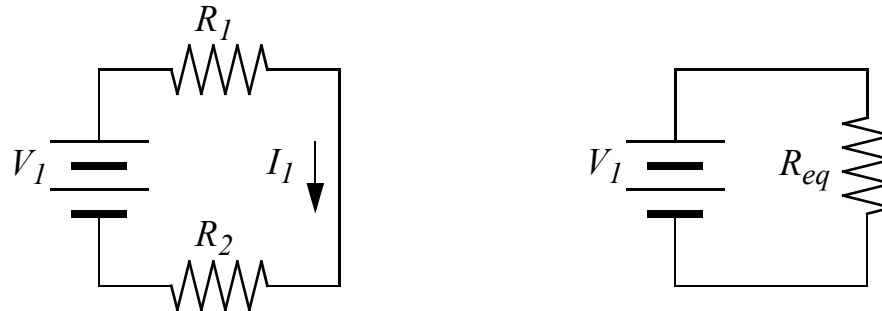In *series* the same current flows through all elements



- Use a one loop application of Kirchoff's voltage law:

$$V_1 = R_1 I_1 + R_2 I_1$$

$$V_1 = (R_1 + R_2) I_1 = R_{eq} I_1$$

$$R_{eq} = R_1 + R_2$$

- In general, the series resistance is the sum of the individual resistances.

Voltage Divider

- The voltage at the point between R_1 and R_2 is given by:


$$V_{out} = I_1 R_2 = \frac{R_2}{R_1 + R_2} V_1$$

- The *voltage divider* is perhaps the most common circuit combination!

Parallel Resistors



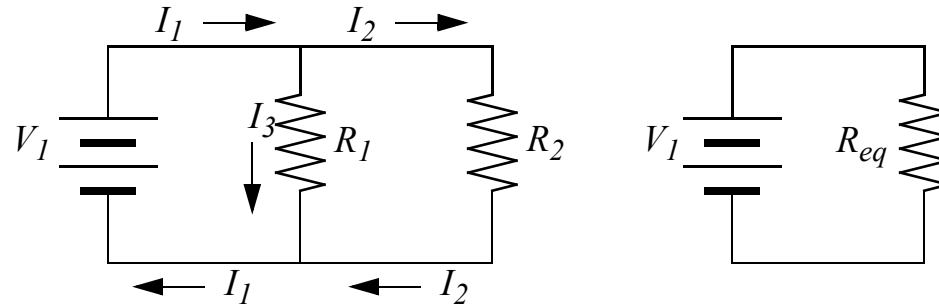In *parallel* the same voltage is present across all elements



- Kirchoff's current law gives: $I_1 = I_2 + I_3$
- There are two loops for Kirchoff's voltage law:

$$V_1 = R_1 I_3 \quad 0 = -R_1 I_3 + R_2 I_2$$

- Eliminate I_3 from the equations, and solve for I_1 :

$$V_1 = R_2 I_2 \quad I_1 = (V_1/R_2) + (V_1/R_1)$$

$$V_1 = \left[\frac{R_1 R_2}{R_1 + R_2} \right] I_1 = R_{eq} I_1$$



- In general, the inverse of the parallel resistance is the sum of the inverse of the individual resistances.

$$R_{eq} = R_1 R_2 / (R_1 + R_2) \quad \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$


Resistor Networks



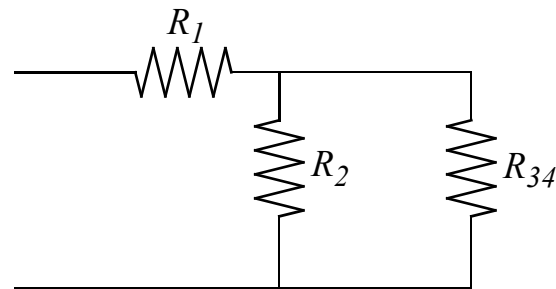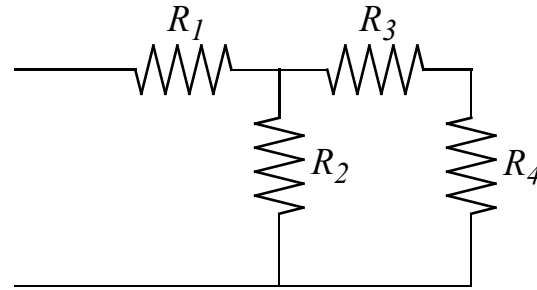- Repeat applications of series or parallel rules as needed:



$$R_{34} = R_3 + R_4$$

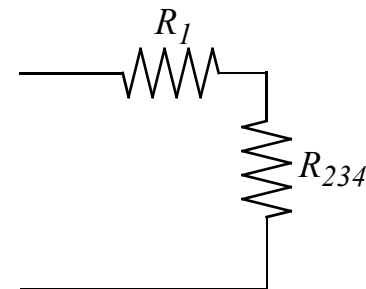

$$R_{234} = \frac{R_2 R_{34}}{R_2 + R_{34}} = \frac{R_2 (R_3 + R_4)}{R_2 + R_3 + R_4}$$


The equivalent network is $R_{eq} = R_1 + \frac{R_2 (R_3 + R_4)}{R_2 + R_3 + R_4}$

V-I Curves




Devices have a characteristic relationship between current and voltage:


- Ohmic device (resistor):

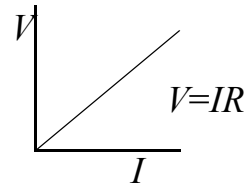


- Voltage source (power supply):

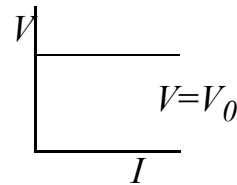

- Current source:

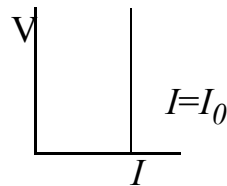

- Battery and resistor in series:

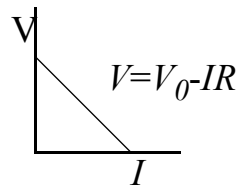


Thevenin's Theorem



Any circuit of batteries and resistors can be reduced to one battery and one resistor in series.

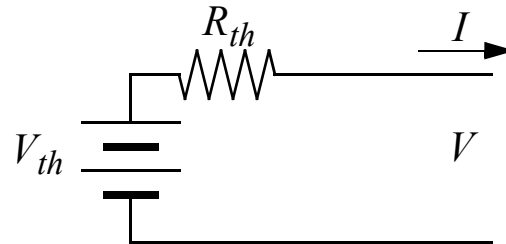- Theorem is based on the linear form of Ohm's law and Kirchoff's laws.
- Any set of circuit equations is reduced to $V(I) = V_{th} - IR_{th}$.




- **Procedure**

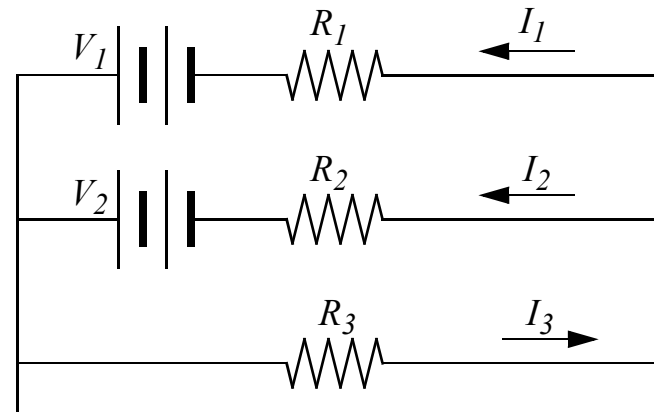1. Find the voltage with no external circuit as V_{th} .
2. Find the current that would flow through an external short circuit.
3. Find the equivalent resistance as $R_{th} = V_{th}/I_{sc}$.

Thevenin Example



- Consider the branch circuit from before, but connect it to an unknown circuit.



$$V_1 = 16 \text{ V}$$


$$V_2 = 6 \text{ V}$$

$$R_1 = 2 \text{ k}\Omega$$

$$R_2 = 4 \text{ k}\Omega$$

$$R_3 = 5 \text{ k}\Omega$$

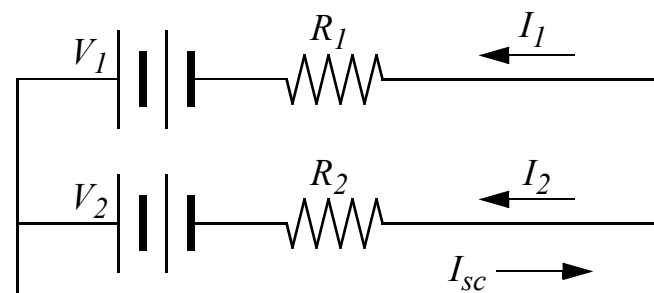- From the Kirchoff example $I_3 = 2 \text{ mA}$. $V_{th} = R_3 I_3 = 10 \text{ V}$
- If the output is short circuited:



$$V_1 = 16 \text{ V}$$

$$V_2 = 6 \text{ V}$$

$$R_1 = 2 \text{ k}\Omega$$

$$R_2 = 4 \text{ k}\Omega$$

$$I_3 = V_1/R_1 + V_2/R_2 = 9.5 \text{ mA}$$

- The R_{th} is the same if all batteries are shorted and resistance measured. $R_{th} = V_{th}/I_{sc} = 1.05 \text{ k}\Omega$

Norton's Theorem




Any circuit of batteries and resistors can be reduced to one current source and one resistor in parallel.

- Electrically equivalent to a Thevenin circuit.

$$R_n = R_{th}$$

$$I_n = I_{sc} = V_{th} / R_{th}$$

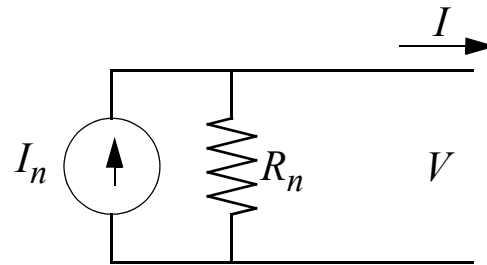

- **Procedure**

1. Find the voltage with no external circuit as V_{th} .
2. Find the current that would flow through an external short circuit I_{sc} .
3. Find the equivalent resistance as $R_n = V_{th}/I_{sc}$.