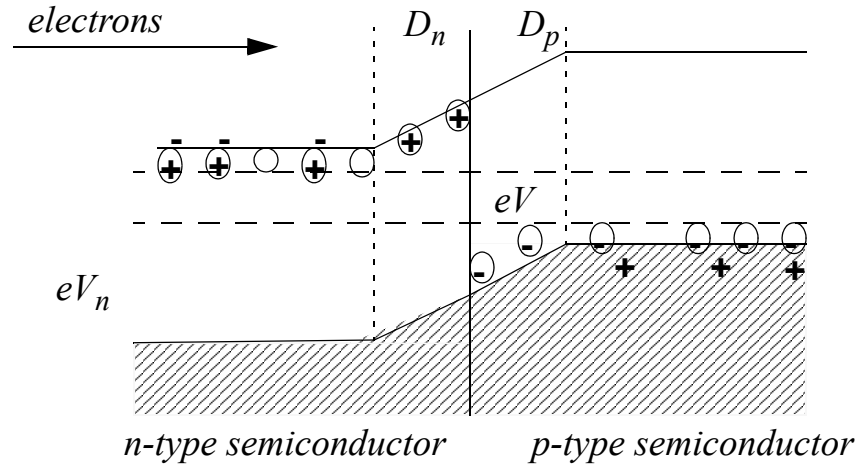


Bipolar Junction Transistors



Diffusion at a p-n Junction

- Forward-biased p-n junction



- Electrons move into p-type material and are picked up by holes.
- Mean free time in the p-type material is related to the density of holes.
- In typical doped silicon $\tau = 10^{-3}$ to 10^{-6} s to recombine, but the time between scattering is about $\tau = 10^{-12}$ s.
- The diffusion time is proportional to the diffusion length squared


$$L \propto \sqrt{\tau}$$

- The mean free path for scattering is about $0.1 \mu\text{m}$, so the mean free path for recombination is about $100 \mu\text{m}$.

Two p-n Junctions



- An n-p-n device has two p-n junctions

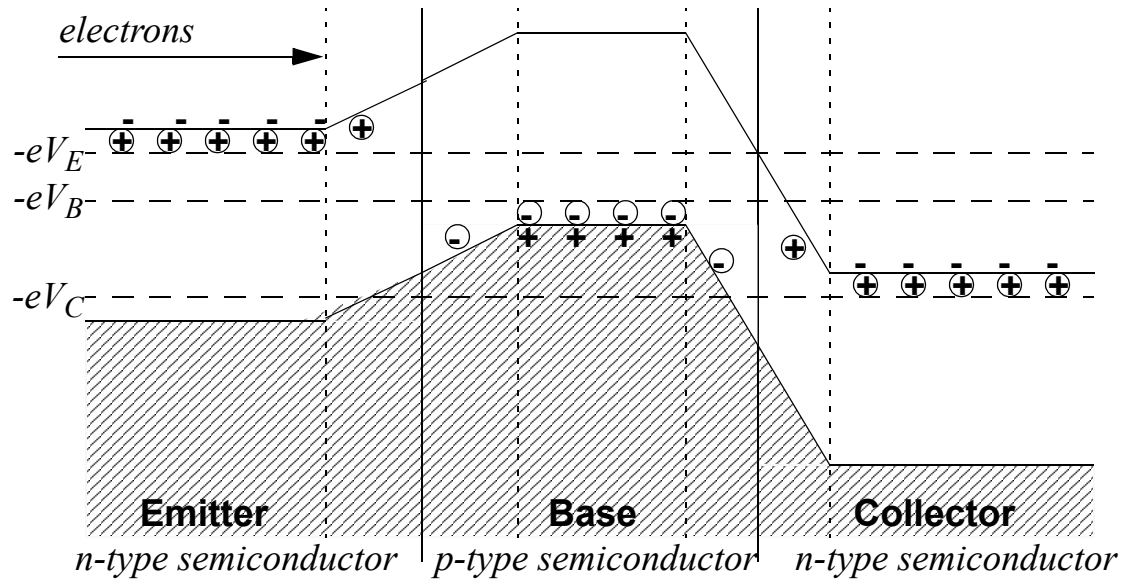

- Electrons in the n-type emitter are at the most negative potential. The first p-n junction is biased so electrons flow into the base. Some electrons will recombine in the base, others make it across the base without recombining.
- The second p-n junction is reverse-biased and has no barrier for electrons flowing from p-type to n-type material.
- Electrons that make it to the collector will immediately enter the collector to continue as current.
- A pnp transistor is very similar except that the current is due to holes.

Current Flow in a BJT




- The current in the collector is proportional to the emitter current reduced by electrons absorbed by the base.

$$I_C = \alpha I_E + I_{CO}$$

α is the fraction of electrons able to get through the base to the collector.

I_{CO} is the reverse current due to the normal base-collector junction, but this is very small.


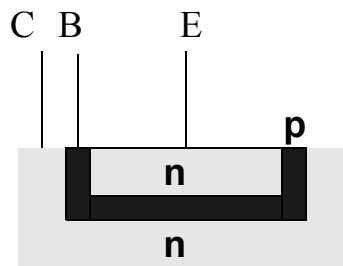
- An ideal junction would have $\alpha = 1$.
Real transistors have $\alpha = 0.95$ to 0.99 .
- α is best for thin bases or lightly doped bases.
- If the base doping is equal to the emitter doping then half the emitter current would be due to base carriers, and α could not exceed 0.5.





BJTs as Circuit Elements



- Schematic symbol:

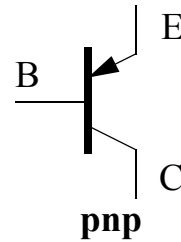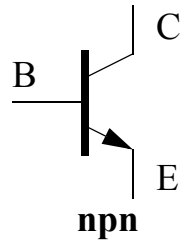


- Transistor biasing:

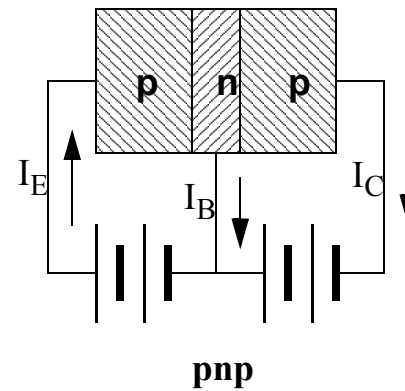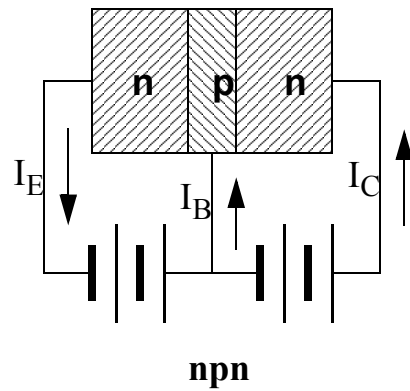

Diode Model



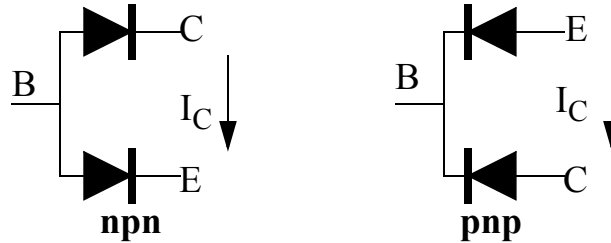- The transistor can be viewed as two diodes



- A transistor can be checked with an ohmmeter
- Forward current I_{BE} is like a diode, exponential I with V over any orders of magnitude
- Typical currents I_C are mA at 0.6 V in Si (0.25 V in Ge)
- V_{CB} is limited by reverse breakdown like a diode: 10-20 V typically.
- Transistor limits $V_{CE\ max}$ and $P_{\max} = I_C V_{CE}$

Collector Current



The collector current I_C is not like a diode!

- Use Kirchoff's law at the junction:

$$I_E = I_B + I_C$$

- Include the effect of carriers through the base:

$$I_E = I_B + \alpha I_E + I_{CO} \cong I_B + \alpha I_E$$

- The relation between base current and emitter current is:

$$I_E = \frac{1}{1 - \alpha} I_B$$


- And the relation between base current and collector current is:

$$I_C = \frac{\alpha}{1 - \alpha} I_B = \beta I_B$$

Current Model



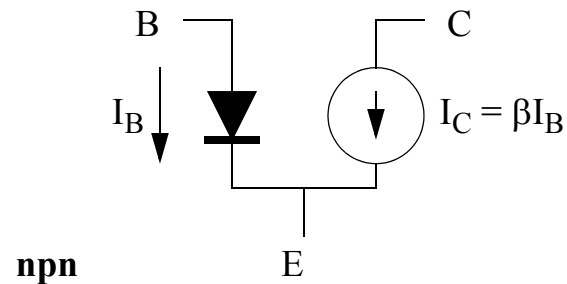- A reverse bias diode looks like a current source/sink until breakdown
- Treat the C-E junction as a current source:




BJT Transistor Rules

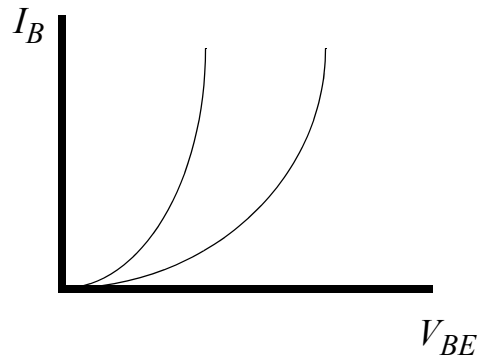1. $V_C > V_E$ (nnp), $V_C < V_E$ (pnp)
2. B-E and B-C junctions are like diodes
3. There are $I_{C \max}$, $I_{B \max}$, and $V_{BE \max}$ like diodes
4. $I_C = \beta I_B = h_{fe} I_B$


Voltage - Current Curves



- Two graphs determine transistor properties.
- Input (V-I for base to emitter) is a typical diode graph
Different curves depend on V_{CE} biasing



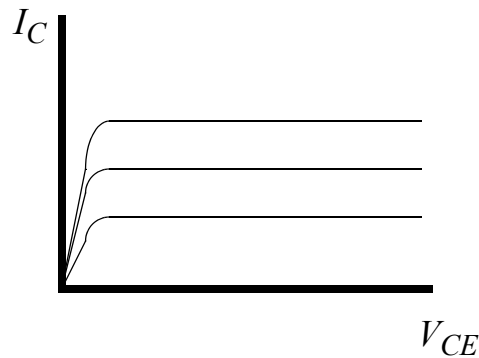- Output (V-I for collector to emitter) looks like a current source
Different curves depend on I_B



- Selecting V_{BE} and V_{CE} determines the behavior of the transistor


Beta Factor



- The relation between base current and collector current is:

$$I_C = \beta I_B$$

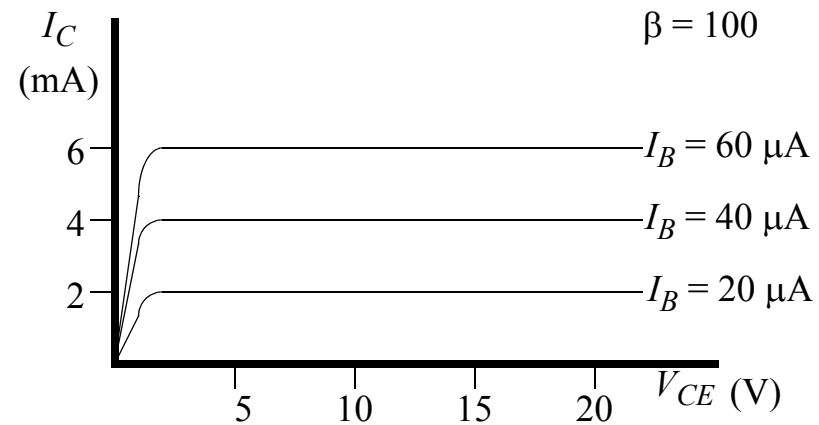- Output transistor curves show the amplification factor β .
- Compare the ratio of I_B to I_C in the region of constant current.




In the above example, as I_B goes from $20 \mu\text{A}$ to $60 \mu\text{A}$, I_C goes from 2 mA to 6 mA . The ratio $4 \text{ mA} / 40 \mu\text{A} = 100 = \beta$.

Common Emitter



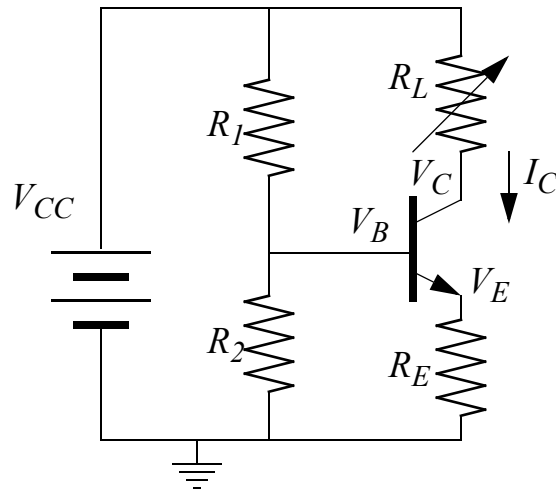- The emitter is in common to input and output.



$$V_C = V_{CC} - I_C R_L$$

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC}$$

$$V_E = I_E R_E \cong I_C R_E$$

- From the transistor rules:


$$V_E = V_B - 0.6V$$

$$I_C = (V_B - 0.6V) / R_E$$


pnp Common Emitter



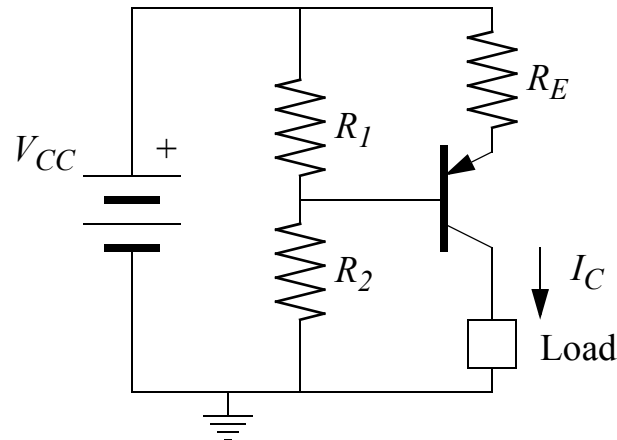- A pnp-transistor is a source of current instead of a current sink.



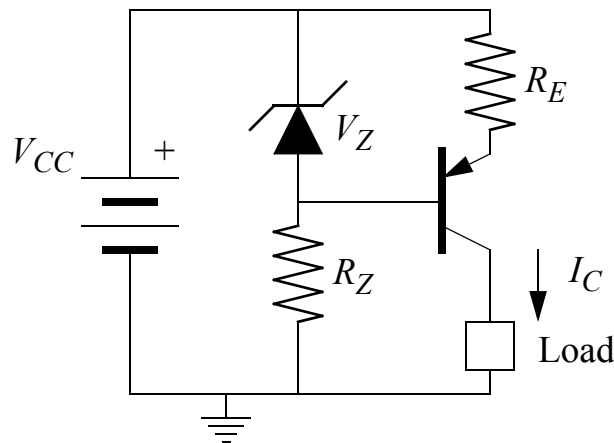- With the pnp the load can be directly attached to ground if the power supply is positive.
- Current sources can also be biased by diodes and zeners.




$$I_C = (V_Z - 0.6V) / R_E$$

Zener Diode Regulation



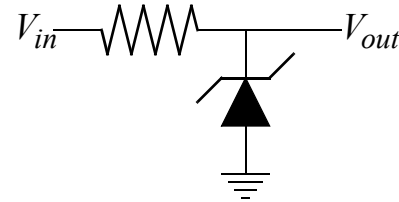- A single zener diode and resistor will regulate voltage:



- Power consumption is based on the current through the zener:

$$P_Z = \left(\frac{V_{in} - V_{out}}{R} - I_{out} \right) V_Z$$

- Consider the following requirements:

$$V_Z = +10 \text{ V,}$$

$$I_{out} < 100 \text{ mA,}$$

$$V_{in} = 20\text{-}25 \text{ V.}$$

The zener needs at least 10 mA to operate :

$$R < (20\text{-}10) \text{ V} / 10 \text{ mA} < 100 \Omega$$




$$P = \left(\frac{25V - 10V}{0.01A} \right) 10V = 3W$$



Common Collector Follower

- Combine a follower and a zener:

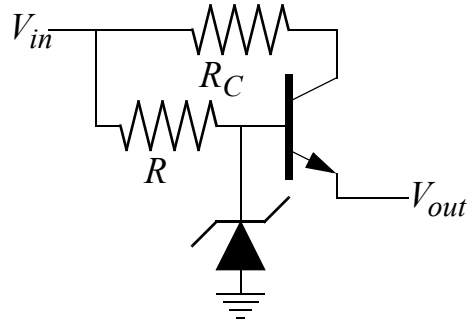

$$V_{out} = V_Z - 0.6V$$

- The current flows through R_C so R can be large and I_Z is small.
- As before, consider $V_Z = +10.6\text{ V}$, $V_{in} = 20\text{-}25\text{ V}$. The zener needs at least 10 mA to operate and $R < (20\text{-}10)\text{ V}/10\text{ mA} < 1\text{ k}\Omega$
- The base current is negligible.

$$P_Z = \left(\frac{25\text{V} - 10.6\text{V}}{680\Omega} - 0\text{mA} \right) 10.6\text{V} = 0.22\text{W}$$

- For the transistor, $I_{out} < 100\text{ mA}$.
- The maximum power dissipation in R_C or the transistor is $P = IV = (0.1\text{ A})(15\text{ V}) = 1.5\text{ W}$