

Logic Gates



A *gate* is a circuit element that operates on a binary signal.

Logic Operations - Boolean Algebra

Logic operations typically have three methods of description:

1. Equation symbol

Typically a mathematical symbol operating on variables, such as

$$A \quad \bar{A} \quad A + B \quad A \bullet B \quad A \oplus B$$

2. Truth table

Lists all possible inputs, followed by the expected output

3. Circuit symbol

Boolean Logic



- Group Properties

$$A \bullet B = B \bullet A$$

$$A + B = B + A$$

$$A \bullet (B + C) = (A \bullet B) + (A \bullet C)$$



- DeMorgan's Theorem

$$\overline{A \bullet B} = \bar{A} + \bar{B}$$


$$\overline{A + B} = \bar{A} \bullet \bar{B}$$

- Unary operations act on a single input.
- Binary operations act on two inputs to produce one output.

Identity




- Identity gate

 

| A_{in} | A_{out} |
|----------|-----------|
| 0 | 0 |
| 1 | 1 |

- Electronic identity

 


Source Follower Buffer

- Buffers have no effect on the logic value in a circuit.

Inverse




- Inverse

 

| A_{in} | \overline{A}_{out} |
|----------|----------------------|
| 0 | 1 |
| 1 | 0 |

- Electronic Inverse

 


Common Source Inverter

- Inverters change a signal from one of two states into the other.
- A circle at the input represents an inverted input.

Logical AND




- AND gate

 

| A_{in} | B_{in} | $A \cdot B_{out}$ |
|----------|----------|-------------------|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

- Electronic AND

 


For V_{out} to be at $+V_{CC}$ both A and B must be within 0.6 V of $+V_{CC}$.

- Disadvantages of this circuit are that a low output is 0.6 V, the output load will be seen by the signal, and the circuit is slow to respond due to the resistor pull-up.

Logical OR




- OR gate

 

| A_{in} | B_{in} | $A+B_{out}$ |
|----------|----------|-------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

- Electronic OR

 


For V_{out} to not be 0 V either A or B must be over 0.6 V.

- Disadvantages of this circuit are that a high output is 0.6 V below the input, the output load will be seen by the signal, and the circuit is slow to respond due to the resistor pull-down.

Not-AND




- NAND gate

 

| A_{in} | B_{in} | $\overline{A \cdot B}_{out}$ |
|----------|----------|------------------------------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

- Electronic NAND

 

- NAND gates can be used to create other logic gates.


$$\overline{\overline{A \cdot B} \cdot \overline{A \cdot B}} = \overline{\overline{A \cdot B}} = A \cdot B$$

$$\overline{\overline{A \cdot A} \cdot \overline{B \cdot B}} = \overline{\overline{A} \cdot \overline{B}} = A + B$$

Not-OR




- NOR gate

 

| A_{in} | B_{in} | $\overline{A+B}_{out}$ |
|----------|----------|------------------------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

 - Electronic NOR (Resistor-Transistor Logic)




- Like NAND, other gates can be made from NOR gates.

Exclusive OR



- XOR gate

 

| A_{in} | B_{in} | $(A \oplus B)_{out}$ |
|----------|----------|----------------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

- The exclusive OR is true if the inputs are different.
- There are a number of equivalent logical constructions for XOR:

$$A \oplus B = (A + B) \cdot \overline{(A \cdot B)}$$

$$A \oplus B = \overline{(\bar{A} \cdot \bar{B})} \cdot \overline{(A \cdot B)}$$

$$A \oplus B = \overline{(\bar{A} \cdot \bar{B})} + (A \cdot B)$$

$$A \oplus B = (A \cdot \bar{B}) + (\bar{A} \cdot B)$$

$$A \oplus B = \overline{\overline{(A \cdot \bar{B})} \cdot \overline{(\bar{A} \cdot B)}}$$

Logic Levels



Boolean Levels

Logic levels are T =True and F =False.

Alternate levels are 1=True and 0=False.



Electronic Levels

Logic levels are H =High and L =Low.

Alternate levels are 1=High and 0=Low.

Positive Logic

- High = TRUE

  



Timing diagram

- High inputs correspond to logical TRUE.

Negative Logic



- High = FALSE

  

- High inputs correspond to logical FALSE.
- A negative logic NAND is equal to a positive logic OR gate.
- By DeMorgan's Theorem:


$$\overline{\overline{A} \cdot \overline{B}} = A + B$$

Note: There can be confusion since in negative logic a logical “1” is not an electrical “1”.

- Negative logic frequently appears in systems where the usual operating point should be HIGH. For example, logic gates may use less current if operated at HIGH.

TTL - Transistor-Transistor Logic

- NAND - 74LS00

 

The diodes and 20 kΩ resistor make a simple AND-gate.

The transistor at Q₁ forms an inverter to the base of Q₂ and Q₄.


The transistors Q₂, Q₃, and Q₄ form a “push-pull” amplifier.

- If *A* and *B* are HIGH, the base of Q₁ is at 5 V, and Q₁ is on. That puts the bases of Q₂ and Q₄ at about 1.4 V turning both on. *V_{out}* is then pulled to ground plus a C-E drop of 0.1 to 0.2 V.
- If *A* or *B* is LOW, the base of Q₁ is at 0.6 V and is off. This holds the base of Q₂ at 5 V and Q₄ at ground. Q₃ is on and *V_{out}* is at 4.4 V. due to a diode drop across the Darlington Q₂Q₃.

CMOS Logic



- NAND 4011B

 

The CMOS MOSFETs are connected as switches.

HIGH at A and B turn on Q_3 and Q_4 while turning off Q_1 and Q_2 .

LOW at A and B turn on Q_1 and Q_2 while turning off Q_3 and Q_4 .

- If both Q_3 and Q_4 are on then V_{out} is at ground, otherwise either Q_1 or Q_2 will be on pulling V_{out} up to V_{DD} .