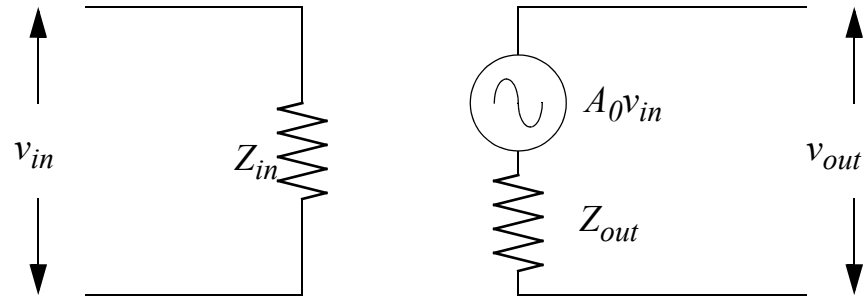



Transistor Amplifiers




- An amplifier is a four connection device
- Voltage amplifier (Thevenin equivalent)



Schematic symbol:

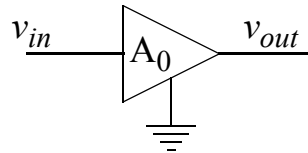

- Current amplifier (Norton equivalent)

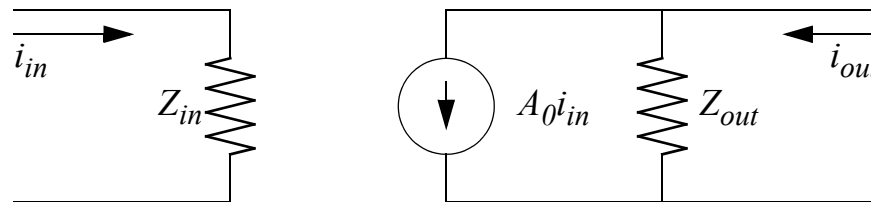


- Amplifiers can also have current in and voltage out or voltage in and current out.

Common Source FET




- DC voltage source

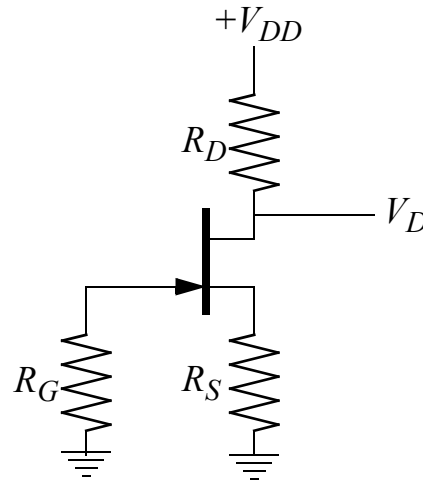

The FET conducts and there is a voltage divider from V_{DD} to ground.

- AC signal

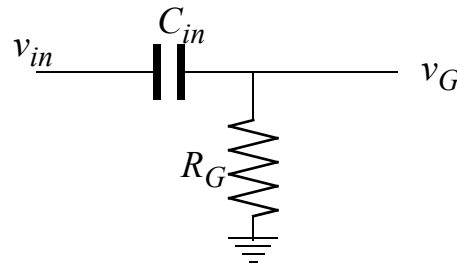


Input forms a high-pass filter.

No DC offset passes into v_G

Common Source Amplifier



- AC voltage amplifier

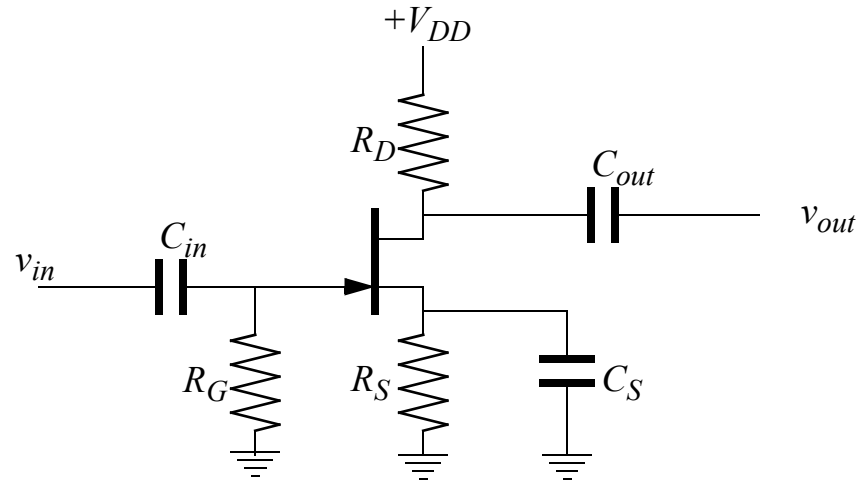

DC separates from AC, $V_{DS} = \text{constant}$.

Forward transconductance g_m is about 10 mS.

$$g_m = \left(\frac{\partial i_D}{\partial v_{GS}} \right)_{V_{DS}} \quad i_D = g_m v_{GS} \quad i_d \cong g_m v_{gs}$$

C_S provides an AC short, so $v_s = 0$, $v_{gs} = v_{in}$.


For the AC signal: $v_{out} = v_d = -i_d R_D$.

- Gain: $A = v_{out}/v_{in} = -g_m v_{gs} R_D / v_{gs} = -g_m R_D$

Common Drain Amplifier



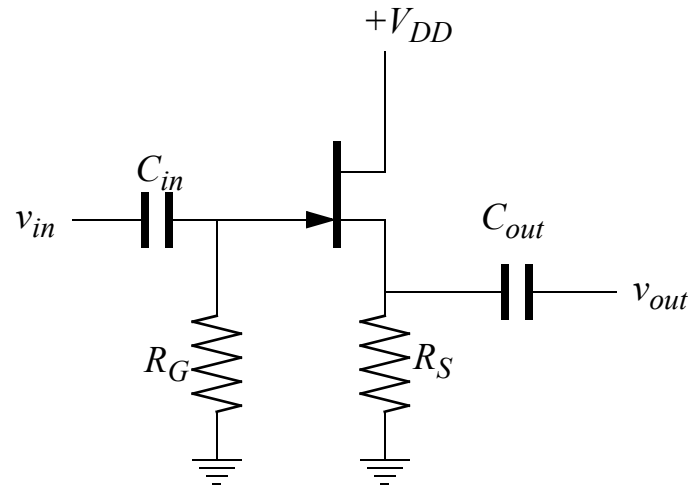- The common drain amplifier takes output at the source



- The input impedance is very high so little current flows into the gate

$$i_g \cong 0 \quad i_s = i_d$$


- The FET has a transconductance g_m :

$$i_d = g_m(v_g - v_s)$$

Source Follower



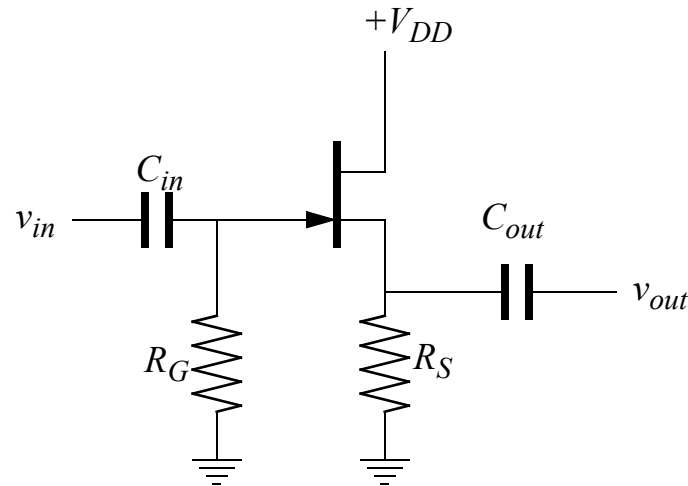- The circuit behaves like a voltage divider



$$v_s = i_s R_S = i_d R_S = R_S g_m (v_g - v_s)$$


$$v_s = \frac{R_S g_m}{1 + R_S g_m} v_g$$

- R_S and $1/g_m$ form a voltage divider, if $g_m = 10 \text{ mS}$, then $1/g_m = 100 \Omega$
- If $R_L \gg 1/g_m$, $v_s = v_g$.
- The AC signal out has the same amplitude as the input - it is a “follower”.

Common Emitter



- The common emitter circuit:

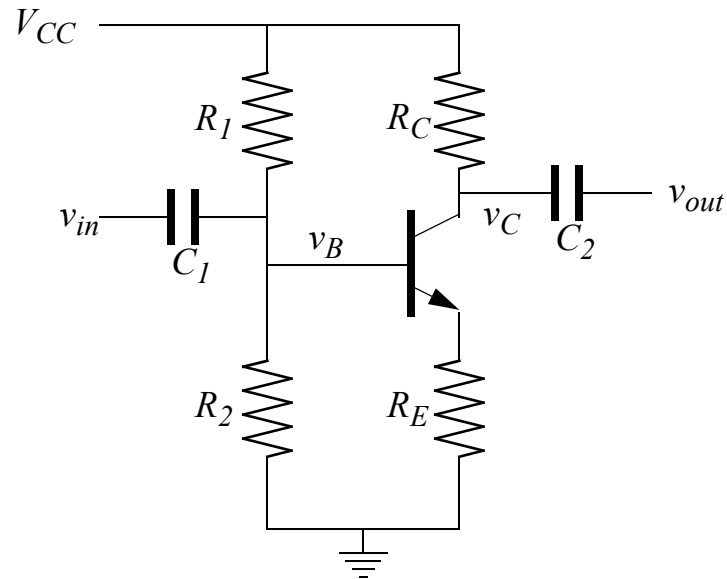

- C_1, C_2 form high-pass filters for the signal, the DC bias remains for the transistor.
- The AC and DC behavior of the transistor can be separated

- Common emitter input is at the base: v_b .

$$v_B = V_B + v_b$$

- Common emitter output is at the collector: v_c .

$$v_C = V_C + v_c$$

Signal Amplification



- The base-emitter junction is like a diode (assume $V_{\text{diode}} = 0.6 \text{ V}$)

$$\begin{aligned}v_B &= V_B + v_b & v_E &= V_E + v_e \\v_B &= v_E + 0.6 & V_B &= V_E + 0.6 \\v_b &= v_e\end{aligned}$$

- The AC part of the emitter current is:

$$i_e = \frac{v_e}{R_E} = \frac{v_b}{R_E}$$

- The AC part of the collector current is:

$$i_c = -\frac{v_c}{R_C}$$

- Since β is large, $i_c = i_e$.

$$\begin{aligned}\frac{v_b}{R_E} &= -\frac{v_c}{R_C} \\v_c &= -\frac{R_C}{R_E} v_b\end{aligned}$$

- This is a voltage amplifier, with gain $A = -R_C / R_E$.
- Negative gain means the output has inverted sign.
- Selecting the gain provides the remaining constraints to select the circuit bias resistors.

Designing an Amplifier



- Select a gain of -10

$$R_C = 10 R_E$$

$$R_E = 230 \Omega$$

$$R_2 = 10R_E + 2 \text{ k}\Omega$$

$$R_2 = 4.3 \text{ k}\Omega$$


$$R_C + R_E = 2.5 \text{ k}\Omega$$

$$R_C = 2.3 \text{ k}\Omega$$

$$R_1 = 48 \text{ k}\Omega - 10R_E$$

$$R_1 = 46 \text{ k}\Omega$$

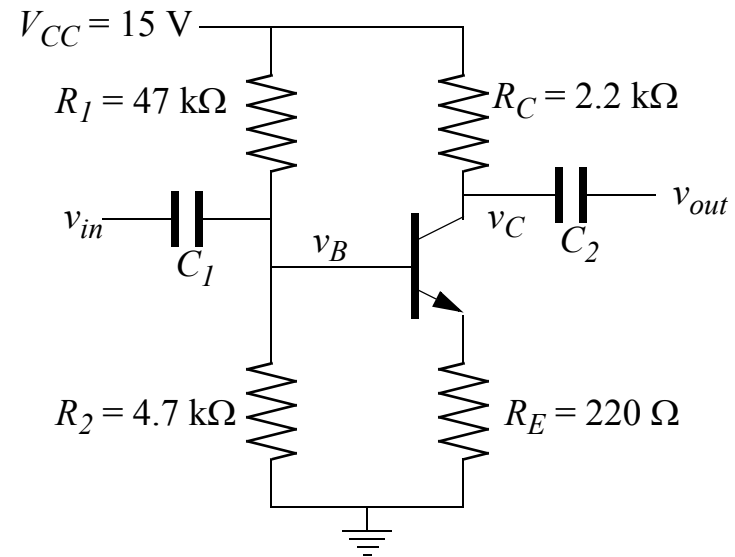- The common emitter circuit with resistances rounded off:



- Double check values:

$$V_B = 1.36 \text{ V}$$

$$V_E = 0.8 \text{ V}$$

$$I_E = 3.5 \text{ mA} = I_C$$

$$V_C = 7.4 \text{ V}$$


$$V_{CE} = 6.6 \text{ V}$$

$$\text{Gain} = -R_C / R_E = -10$$

Emitter Stability



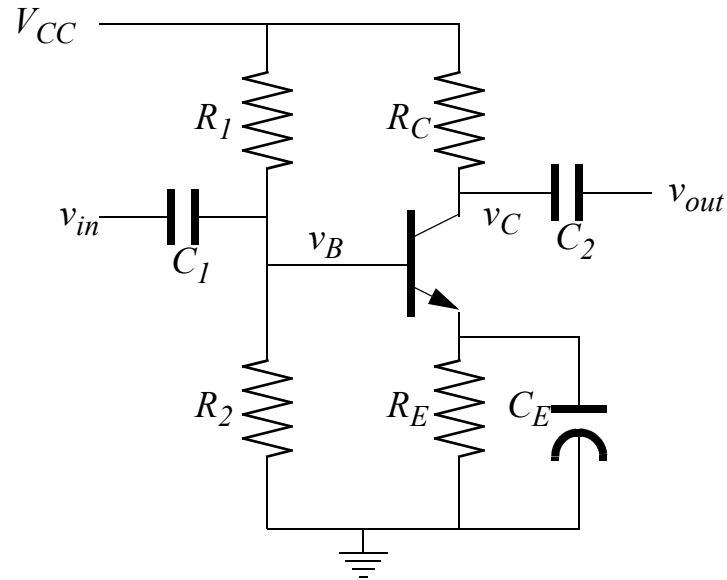- Without an emitter capacitor, the emitter voltage increases with increasing base voltage. This reduces the gain since V_{BE} doesn't increase enough.



- A capacitor C_E in parallel with R_E is a low-pass filter, and should block all signal frequencies.
- Assume for design signal frequencies from 1 kHz to 100 kHz.

$$\omega_b = \frac{1}{R_E C_E} \quad C_E \gg \frac{1}{2\pi f R_E} = 0.69 \mu F$$

- However this also effectively puts v_e at ground, since the capacitor looks like low impedance to AC.

Stabilized Amplifier



- There is a resistance from the base to the emitter that is inversely proportional to the collector current.

$$R_{BE} = \frac{2.6(k\Omega \cdot mA)}{I_C}$$

- The AC part of the base current is:

$$i_b = \frac{v_b}{R_{BE}}$$

- The AC part of the collector current is:

$$i_c = -\frac{v_c}{R_C}$$

- Since $i_c = \beta i_b$:

$$\frac{v_b}{R_{BE}} = -\frac{v_c}{\beta R_C}$$

$$v_c = -\frac{\beta R_C}{R_{BE}} v_b = -\frac{\beta I_C R_C}{2.6V} v_b$$

- This is a voltage amplifier, with gain $A = -\beta I_C R_C / 2.6 V$.
- This gives a gain that is proportional to β for the transistor.