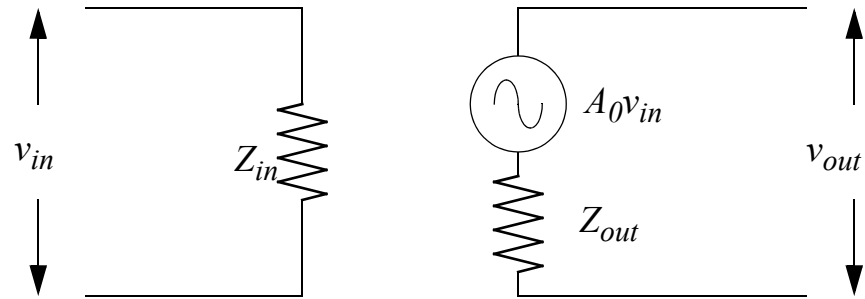



Amplifier Impedance



- Amplifier circuits have impedance at both the input and output.




- AC common emitter

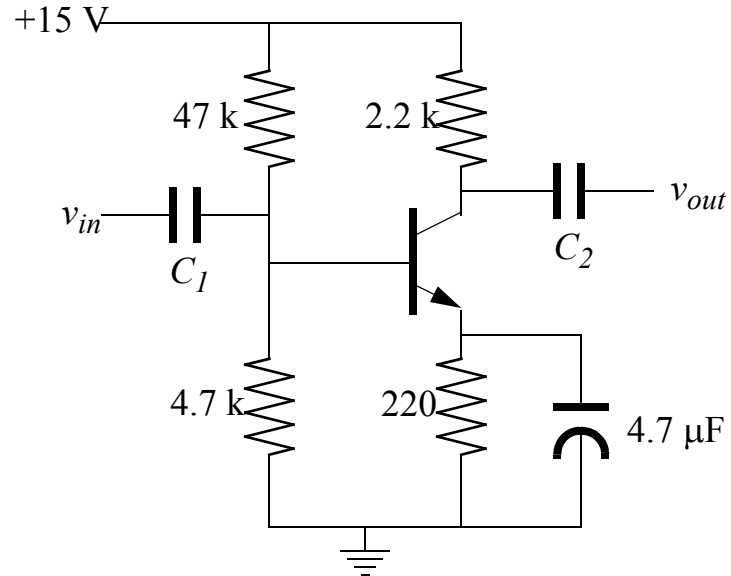

Input Impedance



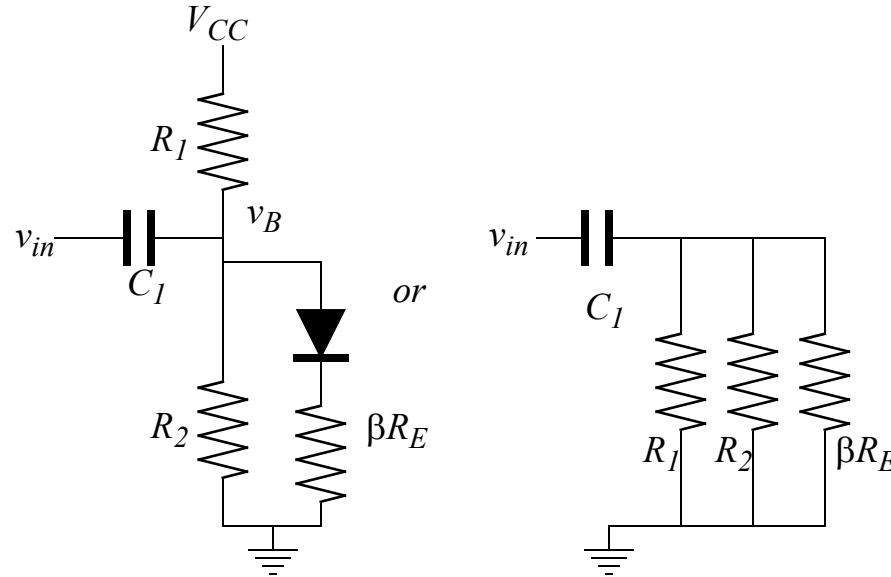- The input signal to a common emitter amplifier sees this circuit:




- This is a high-pass filter with $\omega_b = 1/RC$, where R is the parallel resistance.
- R_E is shorted at high frequency by C_E , but there is an internal resistance of about $2.6 \text{ k}\Omega \text{ mA} / I_C = 870 \Omega$
- For a break frequency of 1 kHz, $R_{in} = 0.71 \text{ k}\Omega$

$$C_1 \gg \frac{1}{2\pi f R_{in}} = 0.22 \mu F$$

Output Impedance



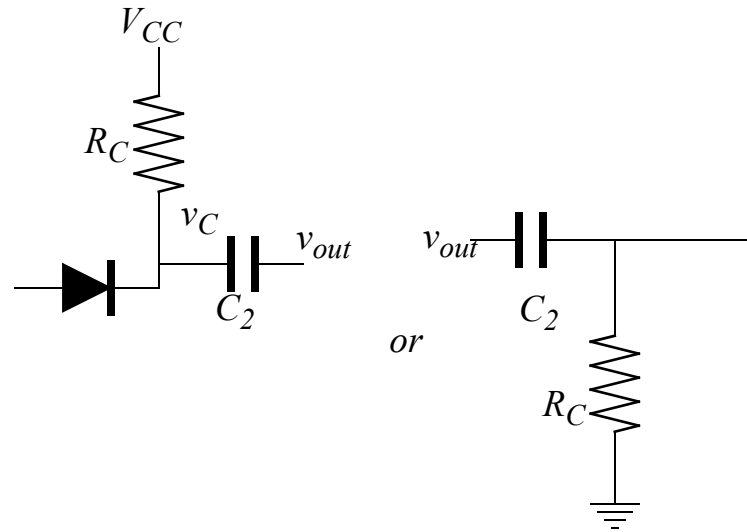- The output signal from a common emitter amplifier sees this circuit:




- This is a high-pass filter with $\omega_b = 1/R_C C_2$

$$C_2 \gg \frac{1}{2\pi f R_C} = 0.069 \mu F$$

Follower Amplifier



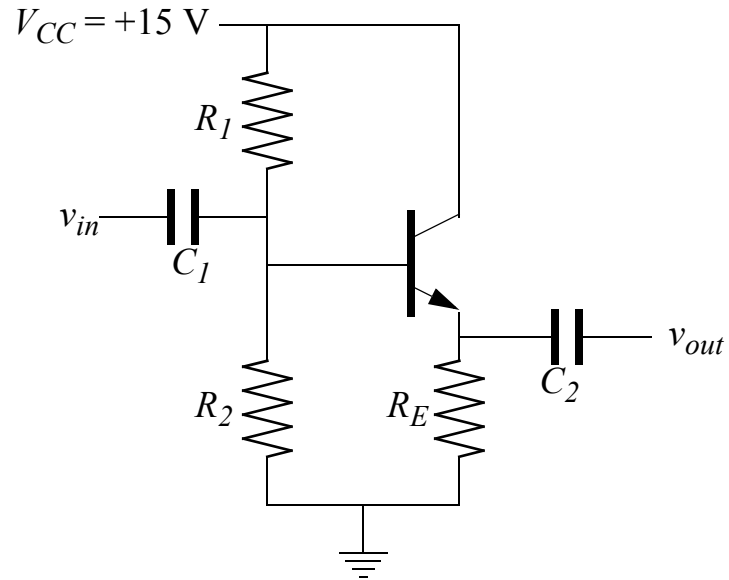- The common collector or emitter follower circuit:



- The emitter is a constant diode drop below the base.

$$v_E = v_B - V_{BE}$$

$$v_e = v_b$$

- The output voltage follows the input.

Design Parameters



- Design for audio, $f = 20 \text{ Hz} - 20 \text{ kHz}$, $I_C = 1 \text{ mA}$.
- Set $V_E = 0.5 V_{CC} = 7.5 \text{ V}$ to have the maximum dynamic range. Set $R_E = V_E / I_C = 7.5 \text{ k}\Omega$.
- Find $V_B = V_E + 0.6 \text{ V} = 8.1 \text{ V}$
- R_1 and R_2 form a voltage divider, $V_B = \frac{R_2}{R_1 + R_2} V_{CC}$ $\frac{R_2}{R_1} = 1.17 = r$
- The impedance due to the base bias should be small compared to the impedance into the base-emitter junction

$$\frac{R_1 R_2}{R_1 + R_2} = \frac{\beta R_E}{10} \quad \frac{10rR_1^2}{(1+r)R_1} = \beta R_E$$

$$R_1 = \frac{\beta R_E (1+r)}{10r} = 139 \text{ k}\Omega \approx 130 \text{ k}\Omega$$

$$R_2 = 162 \text{ k}\Omega \approx 150 \text{ k}\Omega$$


- Total input impedance is $63 \text{ k}\Omega$. Select $C_1 = 0.5 \text{ }\mu\text{F} > 1 / 2\pi f Z_{out} = 0.13 \text{ }\mu\text{F}$.
- Total output impedance $> R_E / 2 = 3.8 \text{ k}\Omega$. Select $C_2 = 4.7 \text{ }\mu\text{F} > 1 / 2\pi f Z_{in} = 2.1 \text{ }\mu\text{F}$.
- The amplifier provides **high input impedance** and **low output impedance**.

Feedback



Generalized Feedback

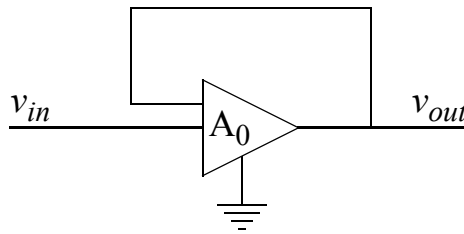- In an amplifier output is a function of input
- It is difficult to design an amplifier with constant gain, and impedance
- Feedback allows the input to be a function of output




Types of Feedback

<u>Sample output</u>	<u>Type of input</u>	<u>Name</u>
Voltage	Voltage	Voltage feedback
Current	Voltage	Current feedback
Voltage	Current	Operational voltage feedback
Current	Current	Operational current feedback

Voltage Feedback



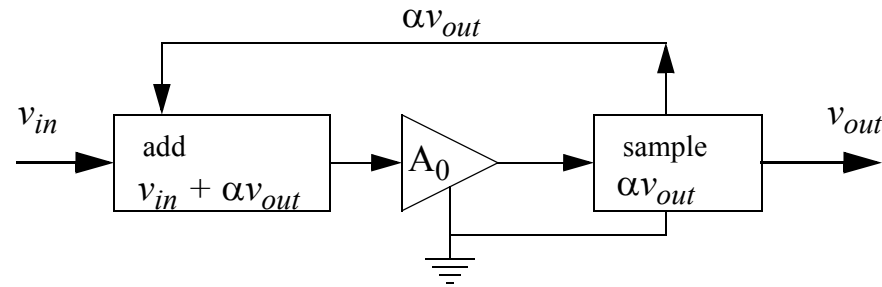- Sample output voltage and add it to input:



- Input to amplifier: $v_{in} + \alpha v_{out}$
- Output of amplifier: $A_0(v_{in} + \alpha v_{out})$
- Output of the circuit:

$$A_0(v_{in} + \alpha v_{out}) - \alpha v_{out}$$

- If A_0 is very large:

$$A_0(v_{in} + \alpha v_{out}) = v_{out}$$

$$A_0 v_{in} = (1 - A_0 \alpha) v_{out}$$

- The effective gain A is:

$$A = \frac{v_{out}}{v_{in}} = \frac{A_0}{(1 - A_0 \alpha)}$$

High Gain



- If αA_0 is near 1: $A = \frac{A_0}{(1 - A_0 \alpha)} \Rightarrow \infty$

But there will be oscillations

- If αA_0 is negative: $A = \frac{A_0}{(1 - A_0 \alpha)} < A_0$
- And if $-\alpha A_0 \gg 1$: $A = \frac{A_0}{(1 - A_0 \alpha)} \cong \frac{1}{|\alpha|}$

Amplifier Stability

- Small changes in gain A_0 affect the effective gain:

$$\frac{dA}{A} = \frac{dA_0}{A_0} - \alpha \frac{dA_0}{(1 - A_0 \alpha)} = \frac{A}{A_0} \frac{dA_0}{A_0}$$

For an amplifier with $A_0 = 1000$, and $\alpha = -0.1$

$$A = 1/|\alpha| = 10, A/A_0 = 0.01$$


100% change in A_0 results in 1% change in A .

Impedance with Feedback



- Input impedance changes with feedback: $Z_{in} = \frac{v_{in}}{i_{in}} = \frac{v_{in0}}{(1 + \alpha A)i_{in}} = \frac{A_0}{A} Z_{in0}$

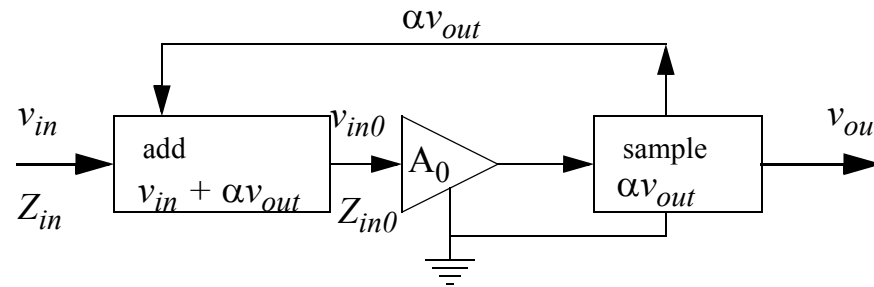
This is an increase for negative feedback



- Output impedance also changes:

$$Z_{out} = \frac{v_{out}}{i_s} = \frac{A v_{in}}{i_s} = \frac{A i_s Z_{out0}}{i_s A_0} = \frac{A}{A_0} Z_{out0}$$


This is a decrease for negative feedback

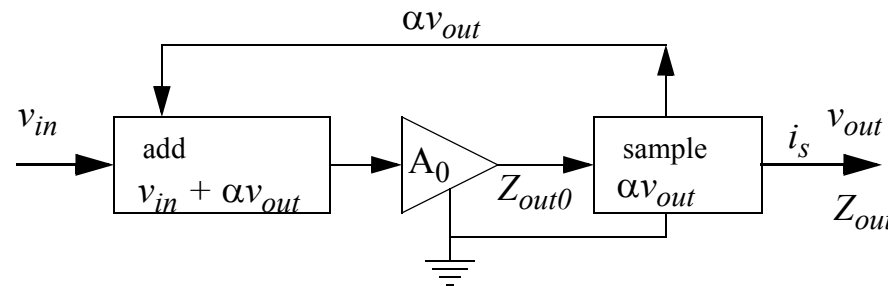

Follower with Feedback



- The emitter follower circuit:

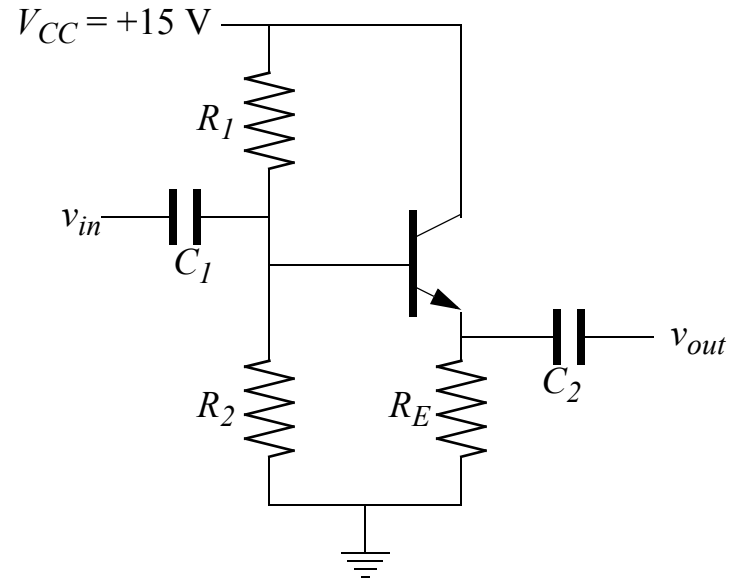

- The base is one diode drop above the emitter, so $v_{be} = 0$.
The feedback voltage exactly cancels the input voltage
 $\alpha = -1$.


$$A = \frac{A_0}{(1 - A_0\alpha)} = \frac{A_0}{(1 + A_0)} \cong 1$$

- The gain $A = 1$ for an emitter follower.

Current Feedback



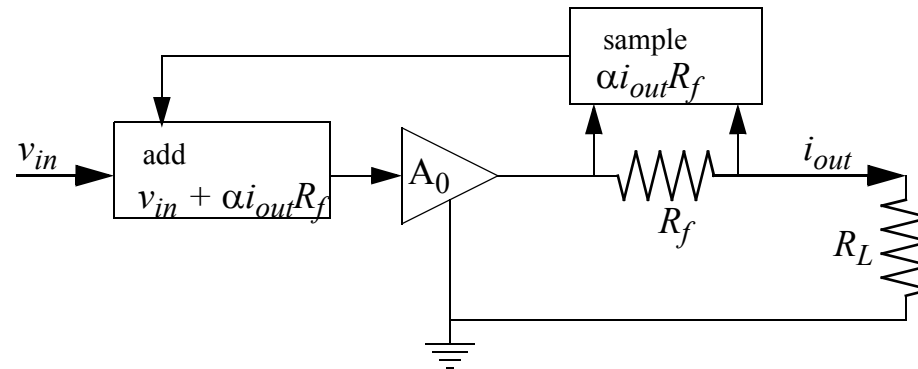- Sample output current, convert to voltage, and add it to input:



- Input to amplifier:

$$v_{in} + \alpha i_{out} R_f$$

- Output of amplifier:

$$A_0(v_{in} + \alpha i_{out} R_f) - i_{out} Z_{out0}$$


- Output of the circuit:

$$i_{out} = \frac{A_0 v_{in}}{R_L + Z_{out0} + (1 - A_0 \alpha) R_f}$$

- If $-A_0 \alpha R_f \gg R_L + Z_{out0} + R_f$ (negative feedback):

$$i_{out} \cong \frac{v_{in}}{-\alpha R_f}$$

Common Emitter with Feedback

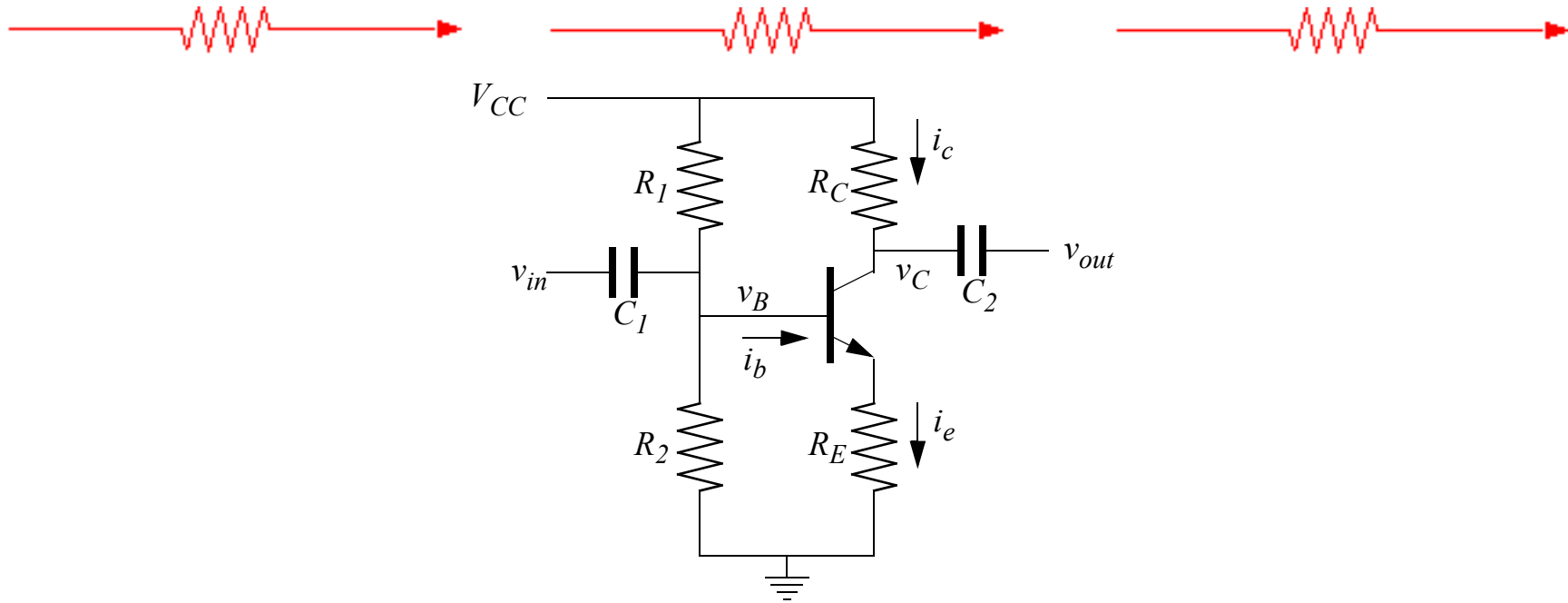

- The feedback is through the emitter

$$v_f = -R_E i_e = R_E i_b - R_E i_b - R_E i_e \quad v_f = -R_E i_b - R_E i_c$$

$$v_f = -R_E i_b + R_E \frac{v_{out}}{R_C}$$

- The two terms correspond to current feedback and voltage feedback.

- The output impedance is $Z_{out} = \frac{v_{th}}{i_s} = \frac{-v_i(R_C/R_E)}{-v_i/R_E} = R_C$