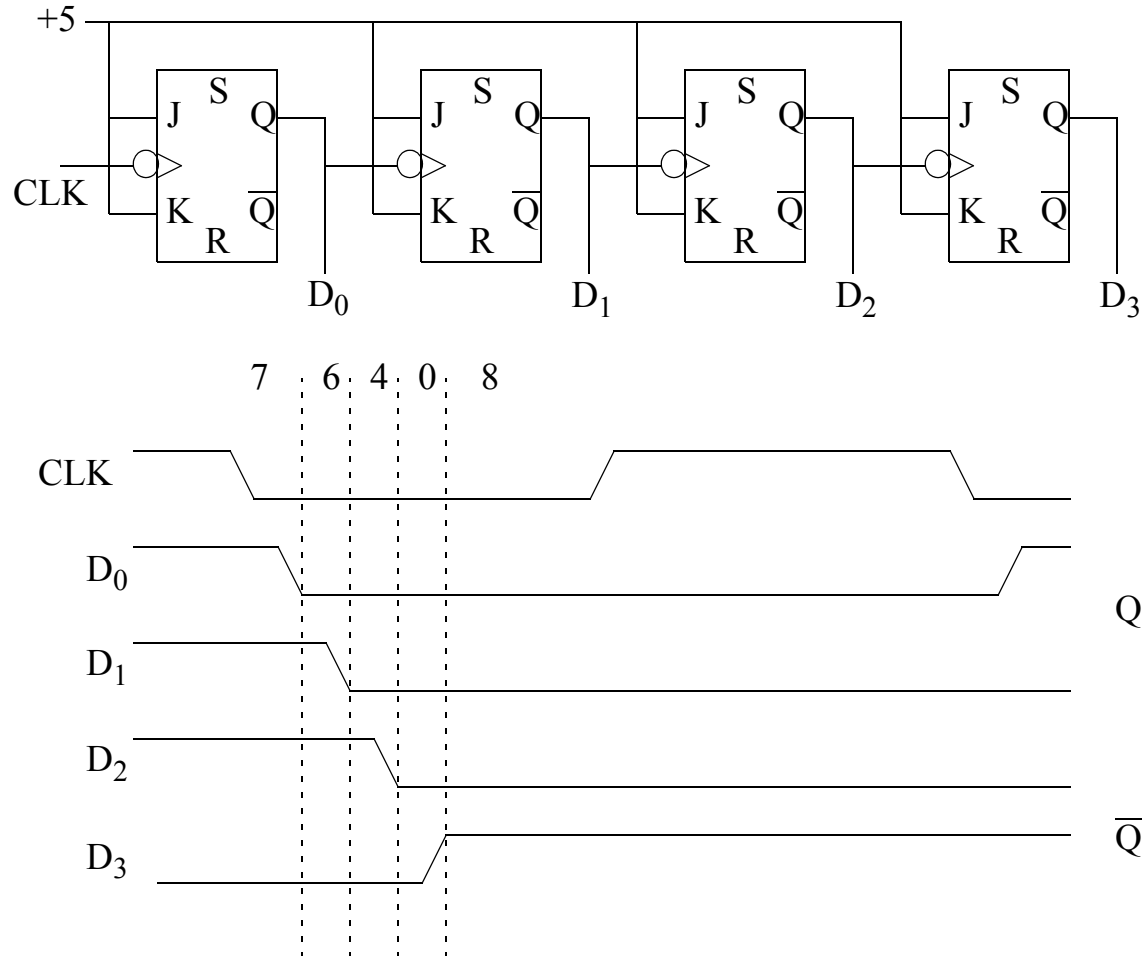


# Counters



## Ripple Counter




In a ripple counter at a clock edge each data bit much change before the next higher bit can change. The apparent counts that exist during the clock transition are called *transients*.

# D-Latch Outputs



- Clock synchronizes output

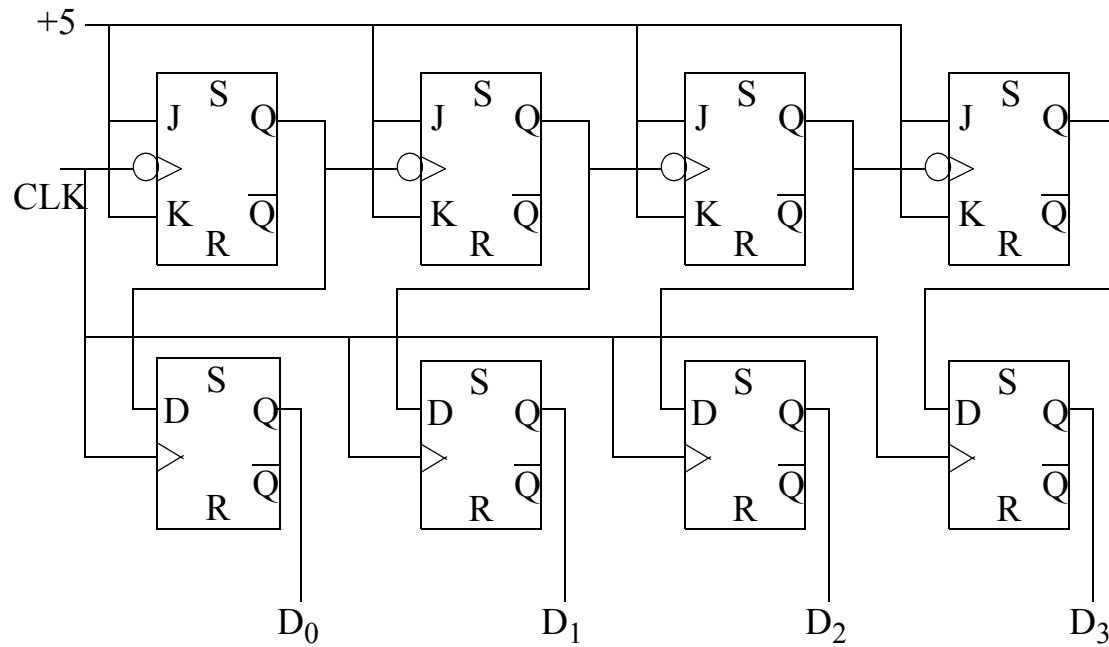


- The ripple counter is updated on the falling edge of the clock.
- The D flip-flops are clocked on the rising edge of the clock, long after the values of all bits are set.
- Transients are suppressed.

# Arbitrary Counter



Count to 10

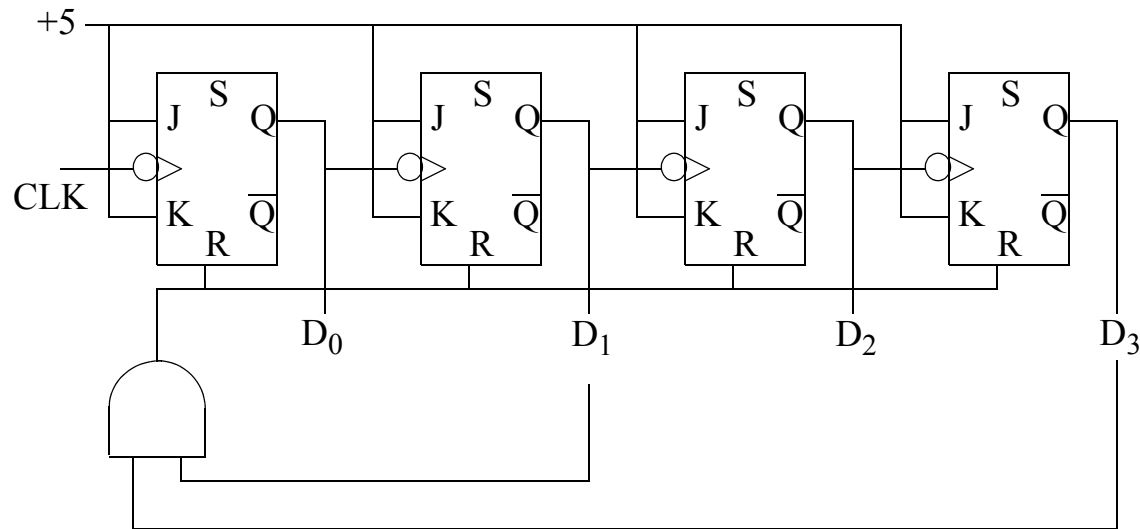

- When the clock causes both  $D_3$  and  $D_1$  to be high, a clear is sent to all flip-flops.
- The first case of this count is at the clock from 9 to 10.

## Load and Clear Inputs

The set and clear of the flip-flops are used in circuits to preload a starting count.


## Latched Outputs

Transient problems can be fixed with output latches.

# Pulse Generator



- Circuit

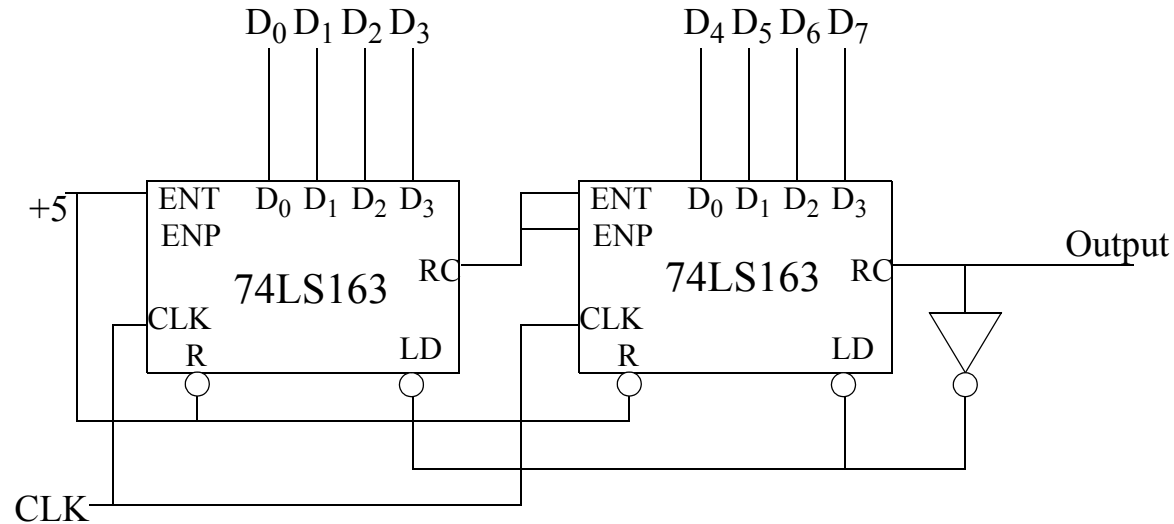

- Each chip has four internal flip-flops.
- ENT and ENP are the JK inputs for the flip-flops.
- $\overline{LD}$  is the  $\overline{SET}$  input for the flip-flops.

The counter is loaded with a value  $x$  from 0-255 (0- $FF_H$ ). With each clock rising edge the count increases by one. When  $FF_H$  is reached, RC goes high. This reloads the counter to repeat the cycle. The output is high for one clock cycle and low for  $256-x$  cycles.


# Synchronous Counters



Clock all flip-flops at the same time.

1. Reduce propagation time
2. Eliminate transient counts

## Divide by $2^n$ (JK)

 

D<sub>0</sub> is dividing the input clock by 2.


D<sub>1</sub> is dividing the input clock by 4. It toggles when D<sub>0</sub> = 1.

D<sub>2</sub> is dividing the input clock by 8. It toggles when D<sub>1</sub> & D<sub>0</sub> = 1.

# Divide By n



- Divide by 3 (D-type)

 

- Divide by 3 Truth Table

CLK	D <sub>0</sub>	Q <sub>0</sub>	D <sub>1</sub>	Q <sub>1</sub>	Count
	0	0	1	0	0
0->1	1	0	0	1	2
0->1	0	1	0	0	1
0->1	0	0	1	0	0
0->1	1	0	0	1	2


# State Diagram



 
## Forbidden States

In the Divide by 3 circuit,  $Q_0 = 1$  and  $Q_1 = 1$  cannot be reached

If it occurs,  $D_0 = 1$  and  $D_1 = 0$  so the next count is 1.



- State diagram for traffic signals

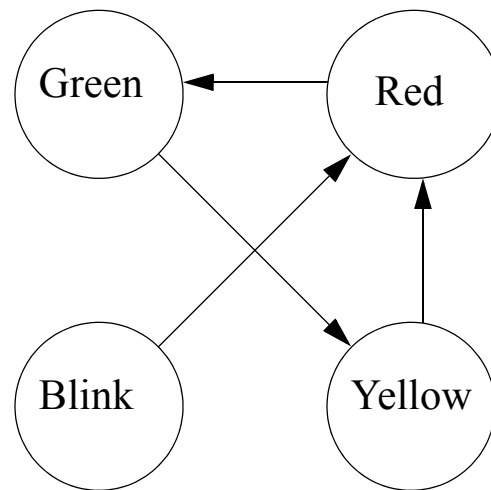

# Registers



## Latches and Registers


- Multiple flip-flops on one IC with one clock and clear
- One output (or output pair  $Q/\bar{Q}$ ) per input
- Designed to “hold” a set of bits

## Transparent Latches

Based on RS flip-flops, these devices pass the input to the output when enabled and hold the output constant when disabled.
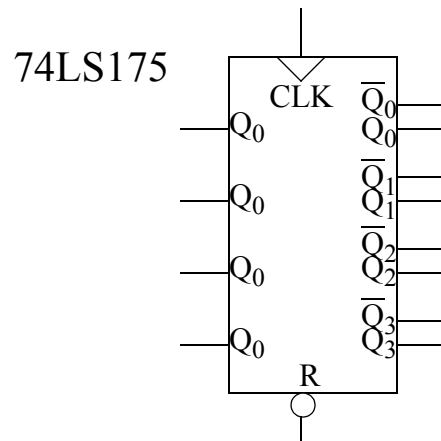
## Type D Registers

Based on D-type flip-flops, these devices transfer the input to the output only on a specified clock edge and then only when enabled. Otherwise the output is held constant.






# Shift Registers



- Serial In/Parallel Out (SIPO)

 


- SIPO Truth Table - bits shift with each clock cycle

CLK	IN	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>
	0	0	0	0	0
0->1	1	1	0	0	0
0->1	1	1	1	0	0
0->1	0	0	1	1	0
0->1	0	0	0	1	1
0->1	0	0	0	0	1

# Parallel Load



- Parallel In/Single Out (PISO)

 


- PISO Truth Table (Data is 0110); LD is parallel load of input data

CLK	LD	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>	OUT
0->1	1	0	1	1	0	0
0->1	0	0	0	1	1	1
0->1	0	0	0	0	1	1
0->1	0	0	0	0	0	0
0->1	0	0	0	0	0	0

# *Shift Register Signal Generators*



- Pseudorandom Noise Generator

 

If the register begins at 0, the input continues to be 0 and there is no change of state.  
If the register begins at 1, that one bit will shift through the register at each clock cycle.  
When it reaches  $Q_6$  and  $Q_7$  then those two clocks will input a 1 instead of a 0 to the input.  
Those two consecutive bits clock through and at the end generate a 101 pattern to the input.  
Only after 255 clock cycles does the number 1 reemerge.

The register generates all values from 1-255 in an arbitrary order that is set by the specific feedback through the XOR gate.

# Truth Table with Feedback



CLK	$Q_0=Q_2@Q_3$	$Q_1$	$Q_2$	$Q_3$	Count
0->1	1	0	0	0	1
0->1	0	1	0	0	2
0->1	0	0	1	0	4
0->1	1	0	0	1	9
0->1	1	1	0	0	3
0->1	0	1	1	0	6
0->1	1	0	1	1	13
0->1	0	1	0	1	10
0->1	1	0	1	0	5
0->1	1	1	0	1	11
0->1	1	1	1	0	7
0->1	1	1	1	1	15
0->1	0	1	1	1	14
0->1	0	0	1	1	12
0->1	0	0	0	1	8

# Feedback Changes



- Feedback  $Q_1@Q_3$

CLK	$Q_0=Q_1@Q_3$	$Q_1$	$Q_2$	$Q_3$	Count
0->1	1	0	0	0	1
0->1	0	1	0	0	2
0->1	1	0	1	0	5
0->1	0	1	0	1	10
0->1	0	0	1	0	4
0->1	0	0	0	1	8
0->1	1	0	0	0	1

This feedback combination does not go through all 15 possible combinations, but only 7.

There are 6 possible feedback choices for 4 bits:

$Q_0 = Q_2@Q_3$  gives 15 numbers;  $Q_0 = Q_1@Q_3$  gives 7 numbers


$Q_0 = Q_0@Q_3$  gives 15 numbers;  $Q_0 = Q_1@Q_2$  gives 7 numbers after 2 is reached

$Q_0 = Q_0@Q_2$  gives 7 numbers after 3 is reached;  $Q_0 = Q_0@Q_1$  gives 3 numbers after 6 is reached

# *Pseudorandom State Diagram*



- Feedback  $Q_1@Q_3$

 

$$Q_0 = Q_1 @ Q_3$$