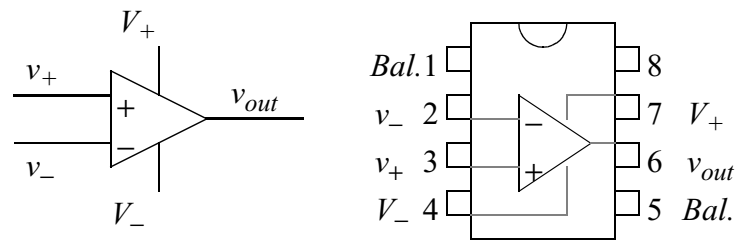


Overview


The purpose of these experiments is to use integrated circuits to generate power sources of fixed DC voltage from unregulated sources.

Components

The TL071 op-amp is an integrated circuit based on JFET technology that comes in an 8-pin dual in-line package (DIP). The connections for the chip looking down with the notch facing up is:



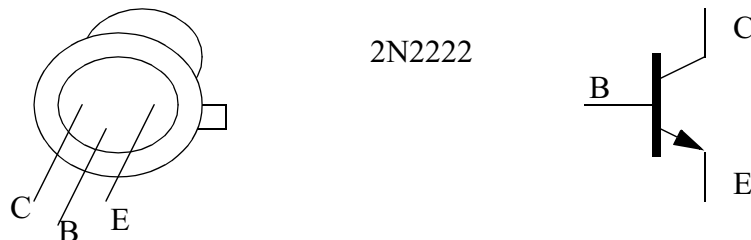The 2N2222 is a general purpose npn transistor. The 2N2222 comes in a TO-18 metal case with leads for emitter, base and collector.




The 2N2222 has maximum ratings as follows:

$$V_{CE} < 40 \text{ V}, V_{CB} < 60 \text{ V}, V_{EB} < 6.0 \text{ V}$$

$$I_C < 0.8 \text{ A}, P = I_C V_{CE} < 1 \text{ W}$$

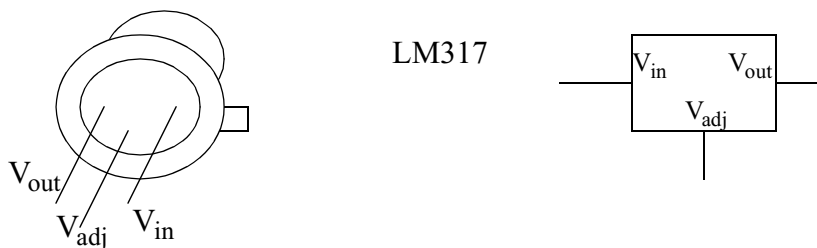The LM317 is 3-terminal adjustable voltage regulator. The LM317 comes in a TO-39 metal case with leads for V_{in} , V_{out} , and V_{adj} .



The LM317 regulates the voltage difference between V_{out} and V_{adj} such that it stays at 1.25 V, as long as $V_{in} > V_{out} + 2 \text{ V}$.

1. DC Supply with Short Circuit Protection

Design a +5 V DC supply based on an op-amp as in figure 1.

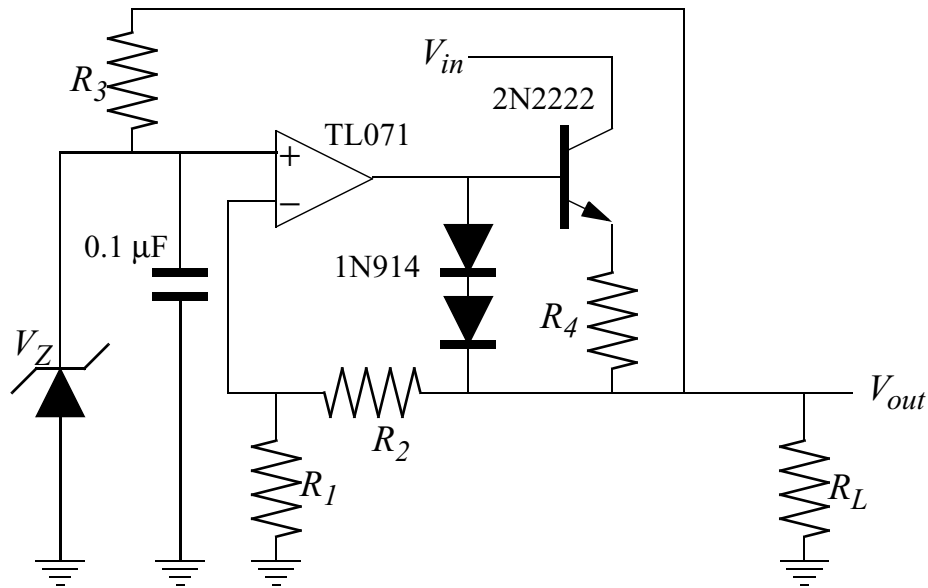


Figure 1: DC Voltage Supply

Begin by identifying the reference voltage for the zener diode V_Z and the maximum current permitted through the transistor I_{Cmax} . Select R_1 and R_2 so that $V_{out} = (1 + R_2/R_1)V_Z$. Select R_3 so that $I_Z = 20$ mA. Select R_4 so that $R_4 > 0.6 \text{ V}/I_{Cmax}$. Use the function generator to create V_{in} with an amplitude of 1 V and a DC offset of 9 V. With $R_L = 100 \text{ k}\Omega$, measure V_{out} with the DMM to get a precise voltage and with the oscilloscope to determine the ripple (in -dB). Repeat the measurement with $R_L = 10 \text{ k}\Omega$, $1 \text{ k}\Omega$, 100Ω , and 22Ω (1W), and compare with a calculated value of I_L . Short R_L with a wire and measure the maximum current.

2. Adjustable Voltage Regulator

Use an LM317 adjustable voltage regulator and 1N4003 diodes to build the circuit in figure 2.

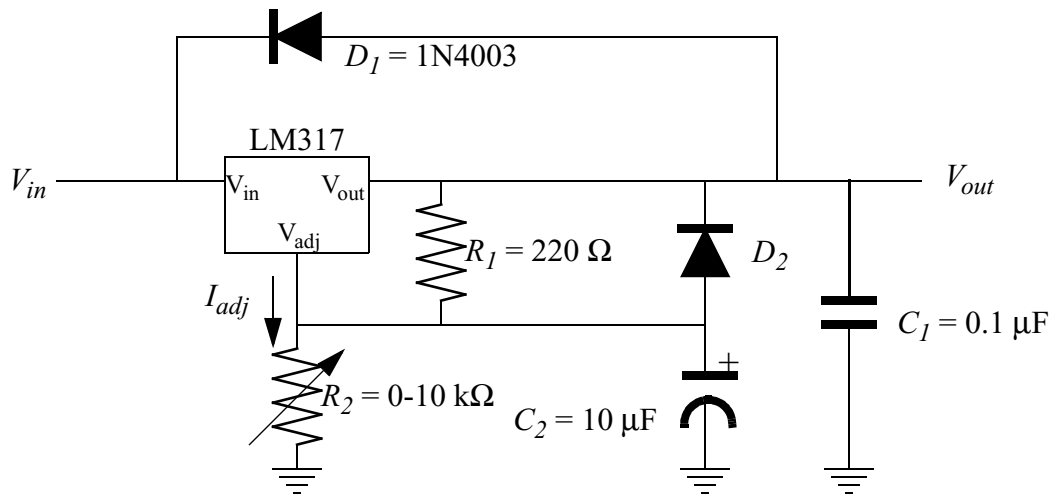


Figure 2: Adjustable Voltage Regulator

The output voltage is given by:

$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{ref} + I_{adj} R_2$$

where $V_{ref} = 1.25$ V.

Use the function generator to provide V_{in} . Vary R_2 to set the output voltage to 5 V. Measure the output voltage and ripple for a variety of load resistors as in part 1. The two diodes are short circuit protection. What short circuits are they specifically protecting against?