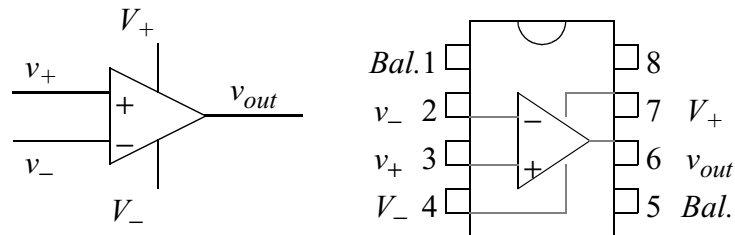


**Overview**


The purpose of these experiments is to study the properties of clocks and square-wave oscillators, both as discrete-component circuits and in integrated circuits (555).

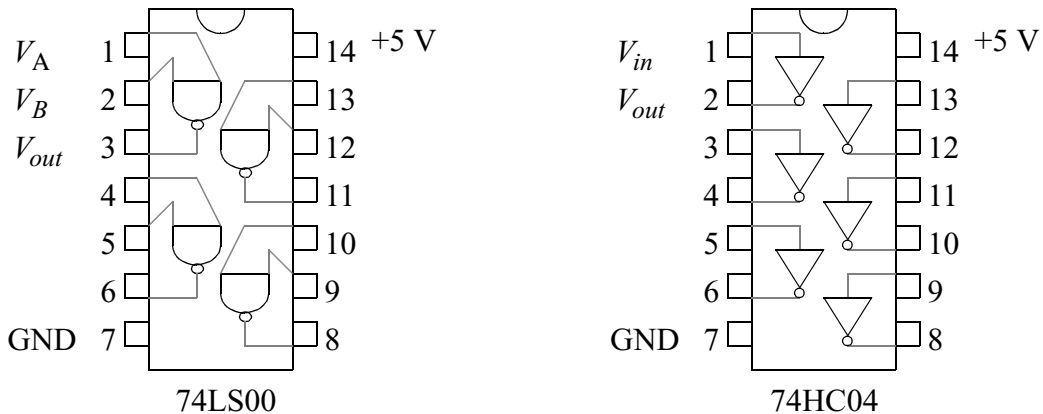**Components**

The CA3140 op-amp is an integrated circuit based with MOSFET inputs to provide a low input bias current. The chip comes in an 8-pin dual in-line package (DIP). The connections for the chip looking down with the notch facing up is:




The 74LS00 is an integrated circuit based on low-power schottky technology that includes 4 NAND gates. The 74HC04 is an integrated circuit based on CMOS technology that includes 6 inverters. The pinouts for the 74LS00 and 74C04 are shown below.



To use any of the gates in the chip, it must be attached to both power (+5 V) and ground.

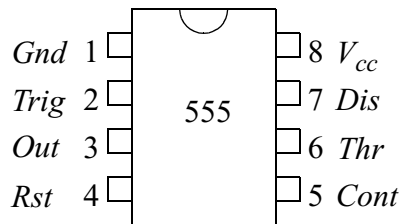The 555 timer is an integrated circuit designed to produce square waves and square pulses between  $Gnd = 0\text{ V}$  and  $+V_{cc}$ . The chip comes in an 8-pin dual in-line package (DIP). The connections for the chip looking down with the notch facing up is:



The *Rst*, pin 4, is an asynchronous reset that operates when it is at ground, and it should be tied to  $+V_{cc}$  for normal operation. The *Cont*, pin 5, is an external control of the internal thresholds, and is normally connected to a  $0.01\ \mu\text{F}$  capacitor to ground. The *Thr*, *Trig*, and *Dis* (pins 2, 6, and 7) are connected to an RC network to establish the clock period, and if necessary to an external trigger for monostable operation.

### 1. Schmitt Trigger

Connect an op-amp without negative feedback to form the circuit in figure 1. Use resistors in the range from 1-10 k $\Omega$ , and use  $V_+ = +5\text{ V}$  and  $V_- = 0\text{ V}$ .

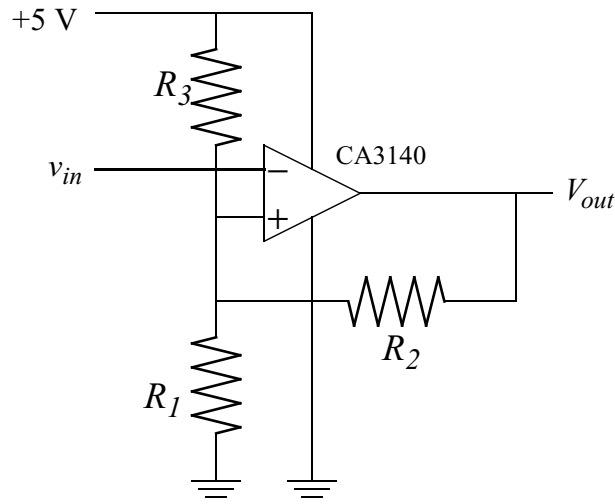


Figure 1: Schmitt Trigger

Set the function generator to provide  $v_{in}$  with a sine wave of 1 kHz and 2.5 V amplitude, and then adjust the DC offset so that the voltage varies from 0 to 5 V. Measure  $V_{out}$  and  $v_{in}$  with the oscilloscope and make a graph of  $V_{out}$  as a function of  $v_{in}$ . Use the X-Y setting of the oscilloscope to view the hysteresis directly. How do the two thresholds compare to the expected value based on the resistors?

## 2. Relaxation Oscillator

Modify the circuit in figure 1 by adding the negative feedback shown in figure 2.

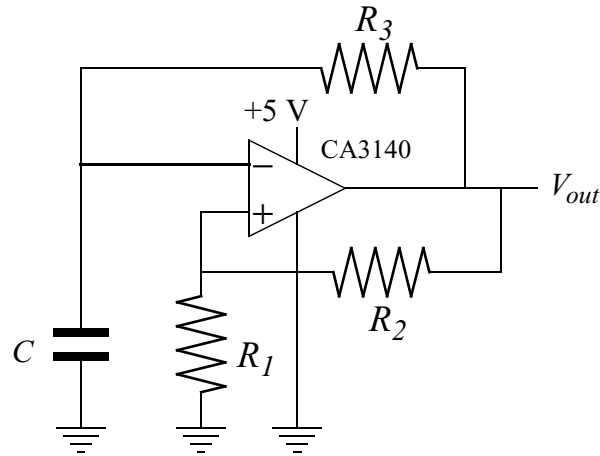


Figure 2: Relaxation Oscillator

Measure the period of oscillation and compare to the time constant  $R_3C$ . Compare the waveform at the output with the waveform at the negative input. How does the threshold voltage at the input compare to the hysteresis limit from part 1?

## 3. Inverter Oscillator

One of the simplest oscillator circuits can be made from two CMOS digital inverters and an RC network as in figure 3.

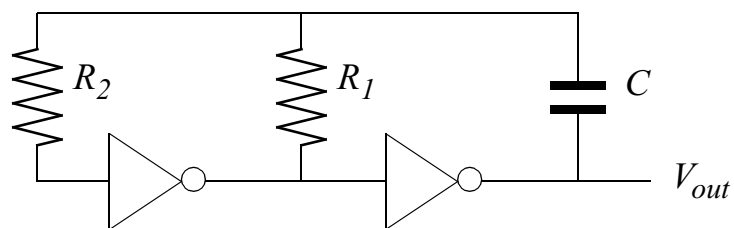


Figure 3: Inverter Oscillator

Set  $R_2 = 0$  and measure the period of oscillation and compare to the time constant  $R_1C$ . Set  $R_2 = 10R_1$  and observe the effect on the oscillation.

#### 4. 555 Monostable Multivibrator

Use a 555 timer and 74HC04 inverter to construct the circuit in Fig. 4. Use  $V_{CC} = +5V$  and use the pulse generator with a 10 KHz square wave as input to the trigger. Start with  $R = 10\text{ K}\Omega$  and  $C = 0.01\ \mu\text{F}$ . Vary the input frequency from 100 Hz to 1 MHz and observe any changes to the output pulse width. Change  $C$  to  $0.001\ \mu\text{F}$ ,  $120\ \text{pF}$  and  $26\ \text{pF}$  to see how short the output pulse can be made. Does the pulse width stay linear with  $RC$ ?

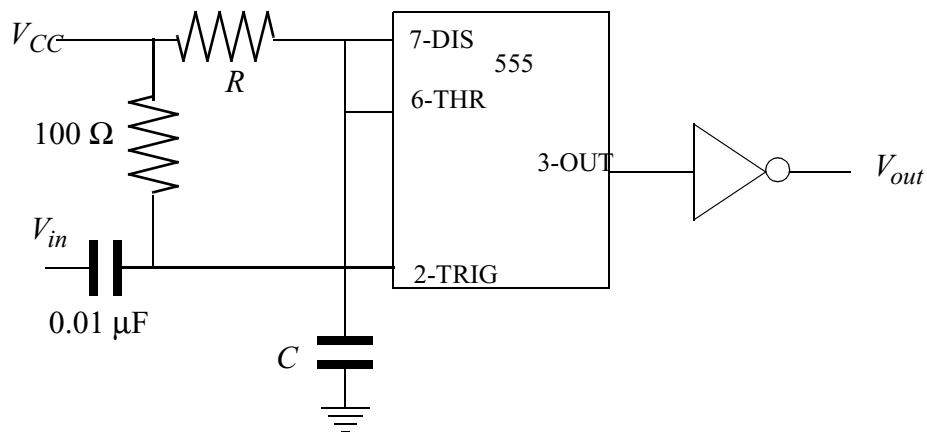


Figure 4: 555 Monostable Multivibrator