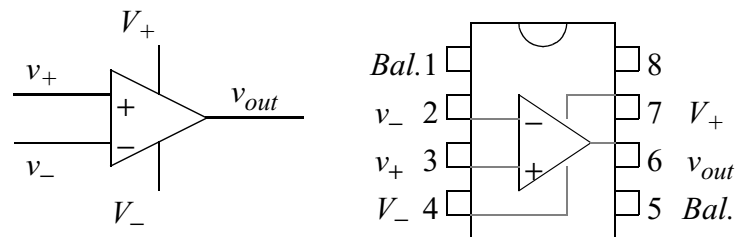


**Overview**


The purpose of these is to use feedback to shift the phase of a signal and to build a circuit that time averages the phase difference to measure the phase.

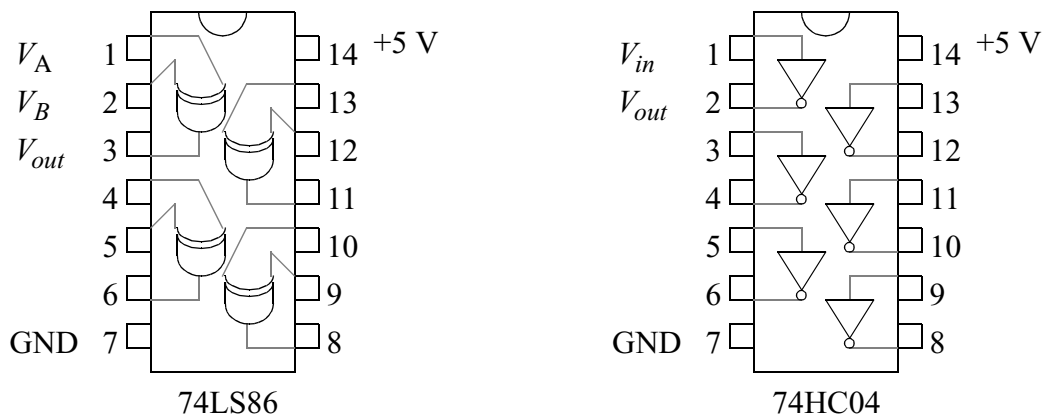**Components**

The TL071 op-amp is an integrated circuit based on JFET inputs and bipolar transistor outputs (BIFET) and comes in an 8-pin dual in-line package (DIP). The connections for the chip looking down with the notch facing up is:



The 74LS86 is an integrated circuit based on low-power schottky technology that includes 4 XOR gates. The 74HC04 is an integrated circuit based on CMOS technology that includes 6 inverters. The pinouts for the 74LS86 and 74HC04 are shown below.



To use any of the gates in the chip, it must be attached to both power (+5 V) and ground.

### 1. Phase Shifting Amplifier

Connect an op-amp to form the circuit in figure 1. Use  $R_1 = R_2 = 10\text{ k}\Omega$  and a  $10\text{ k}\Omega$  potentiometer for  $R$ ; select a capacitor  $C$  so that  $1/RC \ll \omega$ ; and use  $+15\text{ V}$  and  $-15\text{ V}$  for the op-amp power supply.

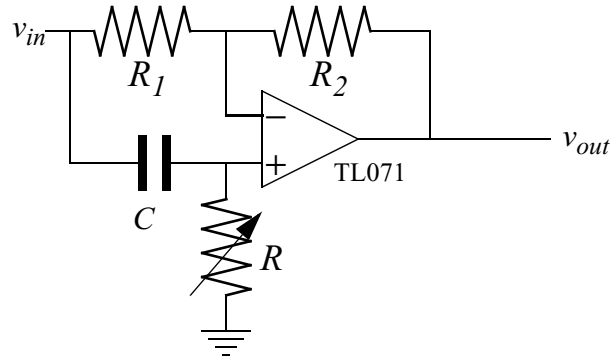


Figure 1: Phase Shifting Amplifier

Set the function generator to provide  $v_{in}$  with a sine wave of  $1\text{ kHz}$  and  $2.5\text{ V}$  amplitude. Measure  $V_{out}$  and  $v_{in}$  with the oscilloscope and make a graph of  $v_{out}$  as a function of  $v_{in}$ . Vary the potentiometer and note the change in phase. Plot  $\phi$  as a function of  $R$ . Use the X-Y setting of the oscilloscope to view the phase difference directly. How does the value of  $R$  compare to  $1/\omega C$  when the phase is  $\pi/2$ ?

## 2. Phase Detector

Modify the circuit in figure 1 by adding additional filters and logic gates as shown in figure 2.

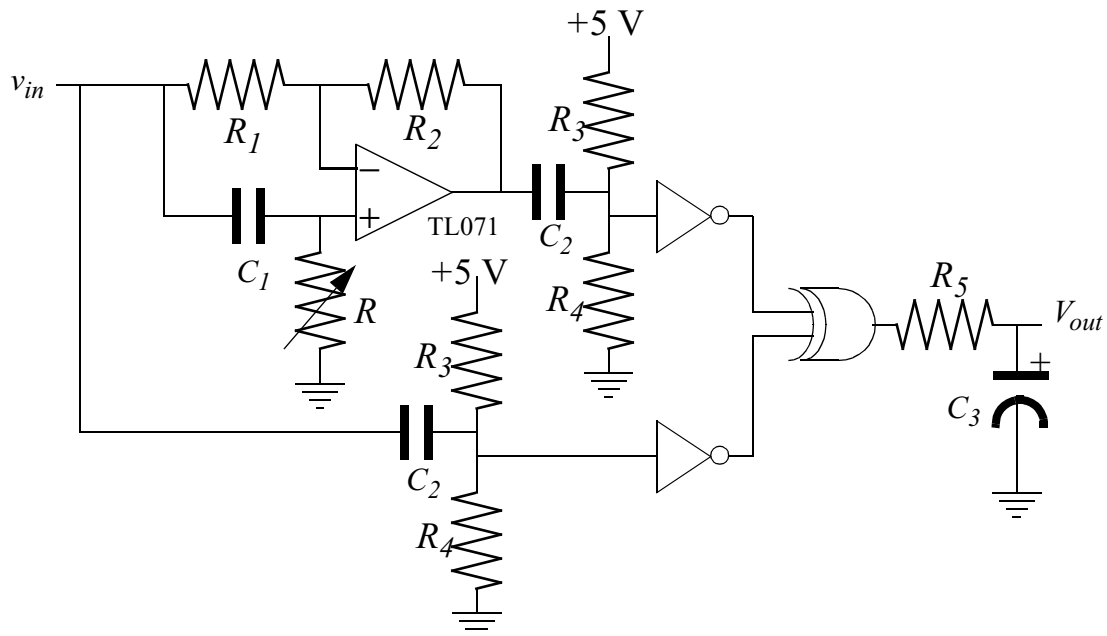


Figure 2: Phase Detector

Use the oscilloscope to observe the signals at the inputs and output of the XOR compared to the  $v_{in}$ . Observe how  $V_{out}$  changes with changing  $R$ . Measure  $V_{out}$  with a DMM and make a plot of  $V_{out}$  as a function of  $R$ . Use the table in part 1 to make a table of  $\phi$  vs.  $R$ .