Physics 475, Laboratory 8 Active Filters

# Overview

The purpose of these is to use feedback to build active analog filters.

### Components

The TL071 op-amp is an integrated circuit based on JFET inputs and biploar transistor outputs (BIFET) and comes in an 8-pin dual in-line package (DIP). The connections for the chip looking down with the notch facing up is:



## Background

Active filters are characterized by their behavior towards gain and phase shift as functions of both the frequency and time. The unity gain Sallen Key active filter is a 2-pole filter with bootstrap-

ping. The break frequency is  $\omega_b = \frac{1}{\sqrt{R_1 C_1 R_2 C_2}}$ and the damping factor is  $d_0 = \frac{1}{Q} = (R_1 + R_2)C_2\omega_b$ .

With a variable gain for negative feedback and matching  $R_1 = R_2 = R$ ,  $C_1 = C_2 = C$ , the gain and damping are independent of the break frequency  $\omega_b = \frac{1}{RC}$ .

$$A_0 = 1 + \frac{R_3}{R_4}$$

$$d_0 = 3 - A_0 = 2 - \frac{R_3}{R_4}$$

As with a mechanical oscillator the gain vs. frequency curve can be described as overdamped  $(d_0^2 > 2)$ ,

underdamped  $(d_0^2 < 2)$ ,

or critically damped  $(d_0^2 = 2)$ .

#### 1. Chebyshev Filter

Connect a TL071 op-amp to form the variable gain Sallen Key circuit in figure 1. Select *R* and *C* such that  $f_b = 1$  kHz. Use a 10 k $\Omega$  potentiometer for  $R_g$  so that  $R_3$  is the feedback part of  $R_g$  and  $R_4$  is the remainder.



Figure 1: Variable Gain Sallen Key Filter

Adjust the potentiometer so that  $d_0 = 0.767$  to provide an underdamped response. Using a sine wave input measure and graph the filter gain and phase shift as a function of frequency. What is the gain roll-off as a function of frequency in dB/octave? Set the function generator to provide  $v_{in}$  with a square wave of 100 Hz. Graph the transient response at the rising edge and note the rise time, overshoot and settling time.

#### 2. Bessel Filter

Adjust the potentiometer for the circuit in part 1 so that  $d_0 = 1.732$  to provide an overdamped response. Repeat the measurements from part 1.