# DC Circuits

- Basic DC circuits consist of resistors and batteries.
- Ohm's law governs the behavior of resistors.

V = IR



• Ohmic devices have a linear voltage - current relationship.



Kirchhoff's Laws -₩₩-• There are two rules that can be applied to circuit analysis.

• Kirchhoff's current rule



• Kirchhoff's voltage rule



### **Branch** Method

- Label a current through each branch of the circuit.
- Set up a set of independent equations for the junctions (current law) and loops (voltage law) in the circuit.



- Current law:  $I_3 = I_1 + I_2$
- Voltage law:

$$V_1 - V_2 = R_1 I_1 - R_2 I_2$$
$$V_2 = R_2 I_2 + R_3 I_3$$

• Solve for *I*<sub>1</sub>, substituting for *I*<sub>3</sub> and *I*<sub>2</sub>:

$$\begin{split} V_2 &= R_2 I_2 + R_3 I_1 + R_3 I_2 \\ V_2 &= R_1 I_1 + V_2 - V_1 + R_3 I_1 + (R_3 / R_2) (R_1 I_1 + V_2 - V_1) \\ R_1 R_2 I_1 + R_2 R_3 I_1 + R_1 R_3 I_1 &= R_2 V_1 + R_3 V_1 - R_3 V_2 \\ I_1 &= (R_2 V_1 + R_3 V_1 - R_3 V_2) / (R_1 R_2 + R_2 R_3 + R_1 R_3) \end{split}$$

• Finally,

$$I_1 = 3 \text{ mA}, I_2 = -1 \text{ mA}, I_3 = 2 \text{ mA}.$$

Load Line



#### **V-I Curves**

• A battery and resistor in series has a characteristic voltage - current graph.





Thevenin Equivalent



- A mu set of sinewite smatters is a decoder of V(D) V UD
- Any set of circuit equations is reduced to  $V(I) = V_{th} IR_{th}$ .



#### Procedure

- 1. Find the voltage with no external circuit as  $V_{th}$ .
- 2. Find the current that would flow through an external short circuit.
- 3. Find the equivalent resistance as  $R_{th} = V_{th}/I_{sc}$ .
- 4. The  $R_{th}$  is the same if all batteries are shorted and resistance measured.

#### Norton's Theorem

• Any circuit of batteries and resistors can be reduced to one current source and one resistor in parallel.

**4-Terminal Circuits** 



• Voltage dividers



- The ratio  $V_{out}/V_{in}$  is the gain A.
- $V_{out} = f(V_{in})$  is the transfer characteristic.



### Diodes



• Diodes permit one-way current flow.



• Diode behavior displayed as a *v*-*i* characteristic



### **Bipolar Junction Transistor**

- The BJT is built like a diode sandwich.
- Quantum properties of the BJT allow for transconductance.



-////

• The emitter follower has the emitter voltage track the base voltage.





**Operational Amplifiers** 

• An op-amp is a difference amplifier with power supplies at  $V_+$  and  $V_-$ .

**→** -----WM-



 $v_{out} = A_0(v_1 - v_2)$ 

• Op amps have special properties when used with negative feedback.



- There are two rules to analyze a circuit with an op amp.
- 1.  $I_+ = I_- = 0$
- 2.  $v_+ v_- = 0$

 $\sim$ 

### Forward Bias Diode



• Consider a single diode with an AC signal.



• A diode will "short-circuit" signals in the forward direction.



• Real diodes are modeled by an equivalent resistance and diode voltage drop.



### **Reverse Bias**



• A diode will block signals in the reverse direction.



• Real diodes pass a small amount of reverse current.



Half-wave Rectifier Ideal behavior doesn't match real behavior. • Forward Reverse Forward  $V_0$ Reverse  $V_0$  $v_{in}$  $v_{in}$  $V_0 - V_D$  $V_0$  $v_{out}$ vout  $-I_0R_{L}$ 1

- Forward voltage is slightly less.
- Reverse current isn't zero.

Full-wave Rectifier

- Two half-have rectifiers in parallel make a full-wave rectifier.
- When  $v_{in}$  is positive the current flows through  $P_1$ ,  $R_L$ , and  $P_2$ .
- When  $v_{in}$  is negative the current flows through  $N_1$ ,  $R_L$ , and  $N_2$ .







If  $v_{in} > 5.6$  V,  $v_{out} = 5.6$  V.

• Two diodes reversed in parallel become a limiter.



If  $v_{in} > 0.6$  V,  $v_{out} = 0.6$  V, if  $v_{in} < -0.6$  V,  $v_{out} = -0.6$  V

#### LABORATORY ELECTRONICS II

## Zener Diode

• Zener diodes have well defined reverse breakdown voltages and allow sufficient current to flow to maintain a constant voltage drop.



If  $v_{\text{in}} > V_Z$ ,  $v_{\text{out}} = V_Z$ .

• Two zeners can be combined to form a limiter.

If 
$$v_{in} > V_Z + V_f$$
,  $v_{out} = V_Z$ , if  $v_{in} < -(V_Z + V_f)$ ,  
 $v_{out} = -(V_Z + V_f)$ 



• The pair of diodes are sold in one package as a transient suppressor.

### **Diode Bias**



• Diodes can bias a circuit to a value other than 0 volts.



- Without the diode this is a high-pass filter.
- With the diode: for  $v_{in} = V_0 \sin \omega t$ ,  $v_{out} = v_{in} + V_0 0.6$  V.

