

AC Circuits




- Pure AC voltage varies in time.

$$v(t) = V_0 \cos \omega t = V_0 e^{j\omega t}$$

- The AC current also varies in time with the same frequency but may have a different phase.
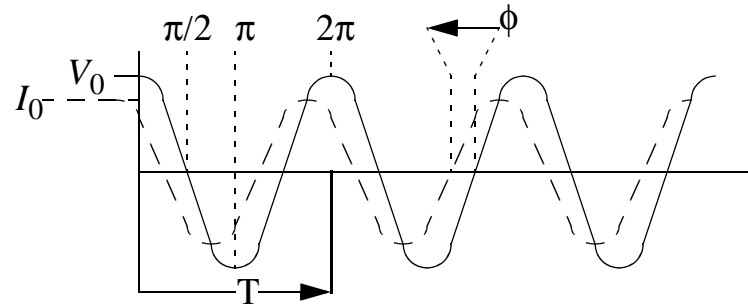
$$i(t) = I_0 \cos(\omega t + \phi) = I_0 e^{j(\omega t + \phi)}$$



- The RMS voltage and current, V_{rms} , I_{rms} , are related to the amplitude.

$$V_{rms} = \sqrt{\langle v^2 \rangle} = \sqrt{\langle V_0^2 \cos^2 \omega t \rangle} = \frac{V_0}{\sqrt{2}}$$


$$I_{rms} = \sqrt{\langle i^2 \rangle} = \sqrt{\langle I_0^2 \cos^2(\omega t + \phi) \rangle} = \frac{I_0}{\sqrt{2}}$$

- The phase doesn't matter for rms measurement.

Phasors



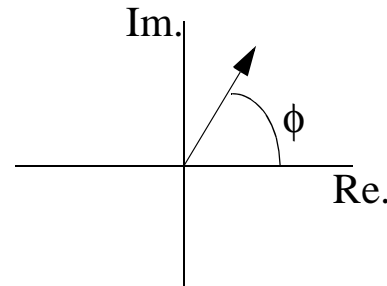- A complex number can be represented as a magnitude and angle in the complex plane.



- The imaginary unit in electronics is j to avoid confusion with current. $j = \sqrt{-1}$
- Euler's formula for an exponential in $j\phi$ links to sinusoidal behavior.

$$e^{j\phi} = \cos \phi + j \sin \phi$$

- Trigonometric formulas can be replaced by exponential ones.


$$\cos \phi = \text{Re}(e^{j\phi})$$

- AC signals are represented by a vector in the complex plane and are called *phasors*.

Capacitors



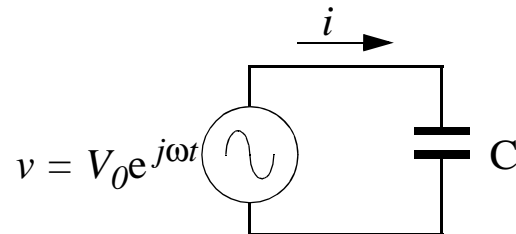- The voltage-current relationship for a capacitor in an AC circuit comes from the stored charge.



$$v = \frac{Q}{C} \quad \frac{dv}{dt} = \frac{i}{C}$$

- For a pure AC signal, there is a simple voltage-current relationship.

$$v = \frac{1}{j\omega C} i$$


- This looks like a complex version of Ohm's law.
- The capacitive reactance is a complex impedance.

$$Z_C = \frac{1}{j\omega C}$$

Inductors



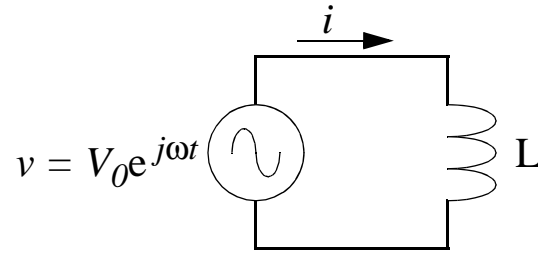- An inductor creates a voltage in response to a changing current.



$$v = L \frac{di}{dt}$$

- This gives rise to another complex current-voltage relationship.

$$v = j\omega Li$$

- The inductive reactance is a complex impedance.


$$Z_L = j\omega L$$

- Capacitive reactances are negative on the imaginary axis and inductive reactances are positive on the imaginary axis.

Gain



- The unit of gain A is the decibel (dB).
- Decibels are a logarithmic measure,
Voltage and current, $A_{\text{dB}} = 20 \log_{10} A$
Power = voltage*current, $A_{\text{dB}} = 10 \log_{10} A$
- There are some useful approximations for amplitude gain.
A factor of 10 is a 20 dB measure
A factor of 2 is about a 6 dB measure
Negative dB is a reduction in magnitude
- A Bode plot displays gain versus the log of the frequency.

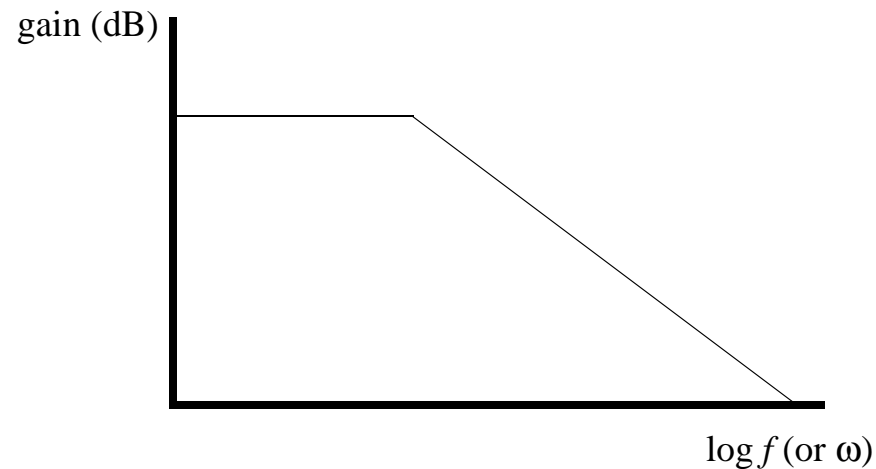

Complex Gain




- The complex gain includes the magnitude of gain and the phase shift.
- The absolute magnitude (a real) is the magnitude of the gain.

$$|A| = |B + jC| = \sqrt{(B + jC)(B - jC)} = \sqrt{B^2 + C^2}$$

- The angle in the complex plane is the phase shift.

$$\tan \phi = C/B$$


- Graphically:

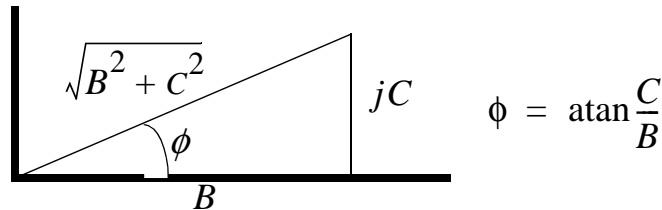

Low-pass Filter



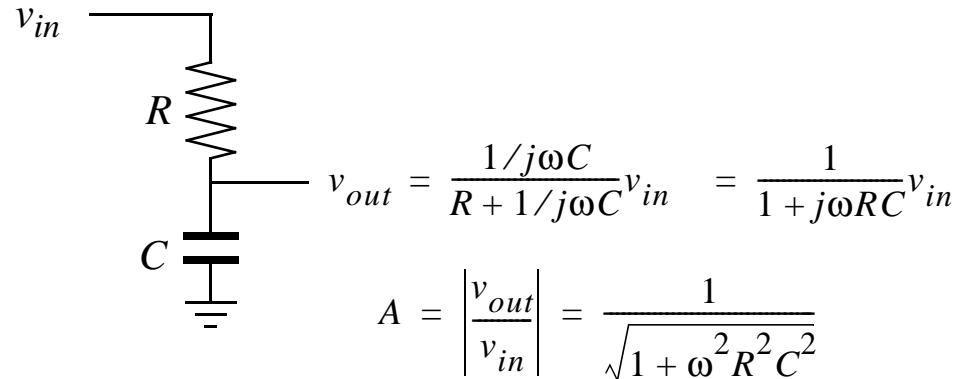- The low-pass filter is a common element in AC circuits.
- It is a voltage divider with complex impedance.



$A = (1 + \omega^2 R^2 C^2)^{-1/2}$; for large ω , A goes as $1/\omega$ or 6 dB/octave.

$\phi = \tan^{-1}(-\omega RC)$; for large ω , ϕ approaches -90° .

Fourier Series



- A periodic signal with a period T can be expressed as $f(t) = f(t + nT)$

- A fourier series represents this as a sum of sine and cosine functions.
- The periodic function can be expressed with $\omega = 2\pi/T$.

$$f(t) = \frac{a_0}{2} + \sum_{n=1}^{\infty} [a_n \cos(n\omega t) + b_n \sin(n\omega t)]$$

- Instead of sines and cosines, the function can be represented in complex notation.

$$f(t) = \sum_{n=-\infty}^{\infty} [c_n e^{jn\omega t}]$$

Fourier Coefficients



- The Fourier coefficients are found by integrating the signal over any one period.
- The first term $a_0/2$ is the DC component of $f(t)$.

$$\int_0^T f(t) dt = \frac{a_0 T}{2}$$

- The coefficients a_n, b_n represent the strength of that frequency component.
- The cosine terms are symmetric and the sine terms are antisymmetric.

$$a_n = \frac{2}{T} \int_{-T/2}^{T/2} f(t) \cos(n\omega t) dt$$

$$b_n = \frac{2}{T} \int_{-T/2}^{T/2} f(t) \sin(n\omega t) dt$$


- The coefficients c_n for the complex form are similar.

$$c_n = \frac{1}{T} \int_{-T/2}^{T/2} f(t) e^{-jn\omega t} dt$$

Square Wave



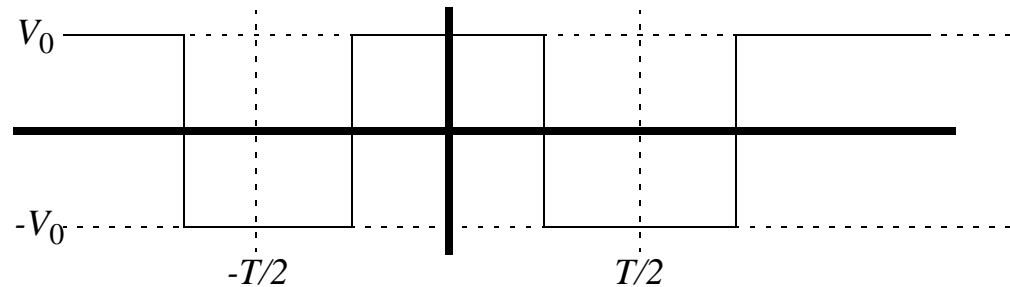- A symmetric square wave can be simply decomposed into a Fourier series.



- The function has been set up as a symmetric function around $t = 0$.
- The period is split into two symmetric halves.

$$v(t) = V_0 \quad -\frac{T}{4} < t < \frac{T}{4}$$

$$v(t) = -V_0 \quad |t| > \frac{T}{4}$$

- Integration can be done on each half separately.

Square Wave Coefficients



- Since the form is symmetric the sine terms will all be 0.

$$b_n = \frac{2}{T} \int_{-T/2}^{T/2} v(t) \sin(n\omega t) dt = 0$$

- The symmetric terms will be 2 times the value of the positive side.

$$a_n = \frac{4}{T} \int_0^{T/4} V_0 \cos(n\omega t) dt + \frac{4}{T} \int_{T/4}^{T/2} -V_0 \cos(n\omega t) dt$$

$$a_n = \frac{4V_0}{Tn\omega} \sin(n\omega T/4) + \frac{4V_0}{Tn\omega} \sin(n\omega T/4)$$

$$a_n = \frac{8V_0}{2\pi n} \sin(2\pi n/4) = \frac{4V_0}{\pi n} \sin(n\pi/2)$$

Low Order Expansion



- Consider the first few terms of the square wave series

$$a_n = \frac{4V_0}{\pi n} \sin\left(\frac{n\pi}{2}\right)$$

$$a_1 = 4V_0/\pi$$


$$a_2 = 0$$

$$a_3 = 4V_0/3\pi$$


$$a_4 = 0$$

$$a_5 = 4V_0/5\pi$$

$$a_6 = 0$$

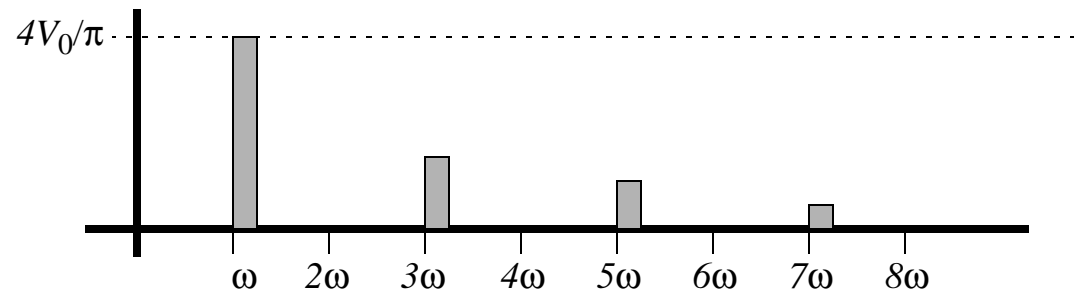

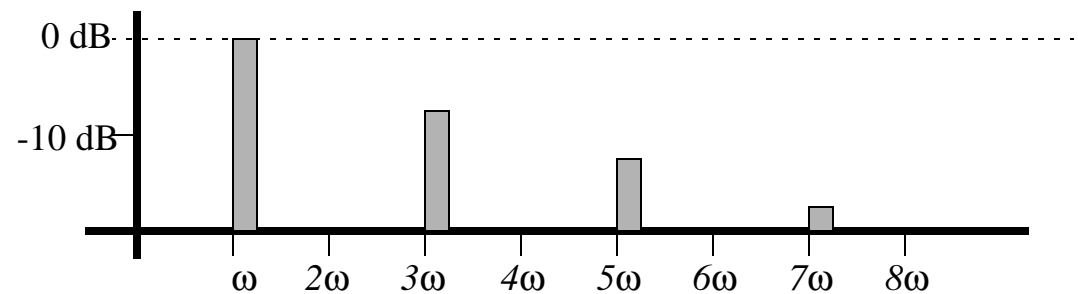
- The signal can be displayed in terms of the frequencies and strengths.



Bridge Circuits



- The Wheatstone bridge is a DC circuit.

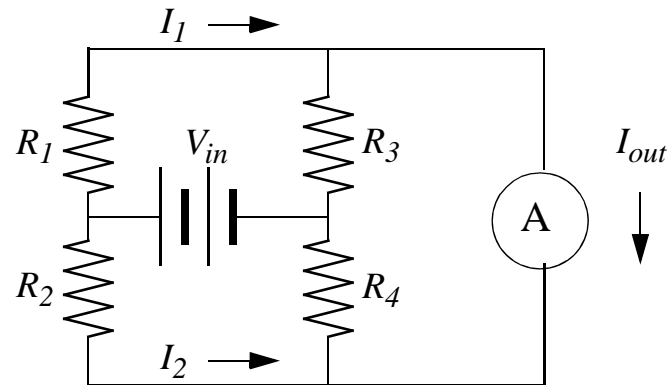

- If the current meter shows $I_{out} = 0$, there are two balance equations.

$$I_1 R_1 = I_2 R_2 \quad I_1 R_3 = I_2 R_4$$


- These can be combined and R_4 can be found in terms of the other resistors.

$$R_4 = R_2 R_3 / R_1$$

Bridge Circuits



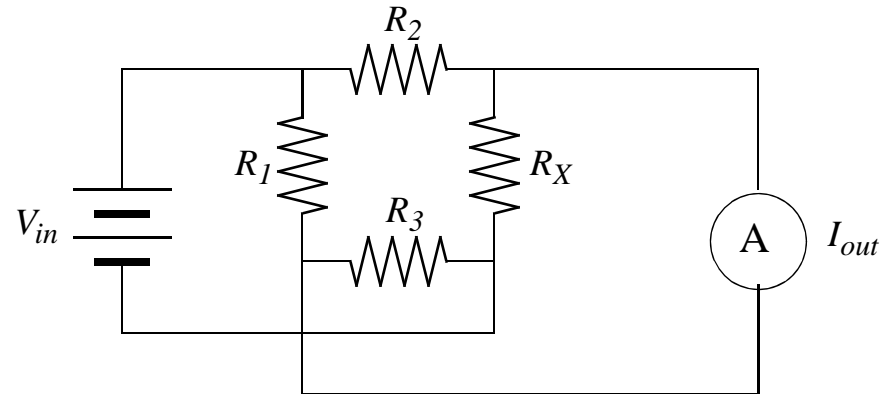- The Wheatstone bridge is typically used to measure an unknown resistance R_X .



- If the user balances the current meter until $I_{out} = 0$.
- The unknown resistance comes from the balance equation.

$$R_X = R_2 R_3 / R_1$$


Op-Amp Bridge

- An op-amp can be used to generate a balance condition.
- Negative feedback sets the voltages on the input of the op-amp.

$$V_{inv} = V_{non} = V_{in} - I_1 R_{i1} = I_2 R_{i2}$$

- The resistor network sets the voltage on the output of the op-amp.
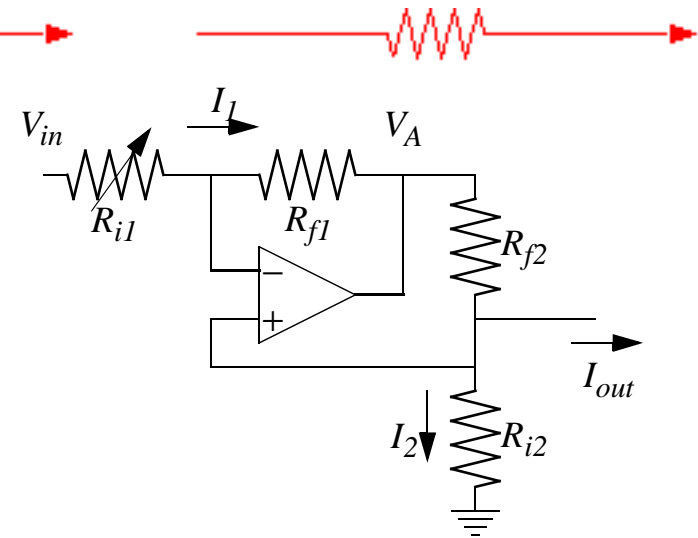
$$V_A = V_{in} - I_1 R_{i1} - I_1 R_{f1} = (I_2 + I_{out}) R_{f2} + I_2 R_{i2}$$



- The variable resistor can be adjusted until the resistors meet the following ratio: $\frac{R_{f2}}{R_{f1}} = \frac{R_{i2}}{R_{i1}}$
- The current only depends on R_{i2} and V_{in} .


$$I_{out} = -\frac{V_{in}}{R_{i2}}$$

- Measuring the current gives the value of the resistor R_{i2} .

AC Bridges



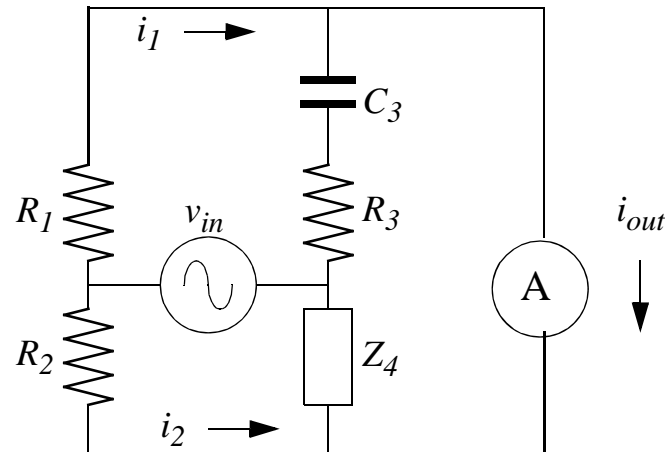- A DC bridge can be modified to measure complex impedances



- Match the real and imaginary parts at $Z_4 = a + jb$.

$$R_1(a + jb) = R_2(R_3 - j/\omega C_3)$$

- The imaginary part measures the capacitance or inductance.

$$b = -R_2/\omega R_1 C_3$$

- The real part measures any intrinsic resistance; and can be used to calculate the Q.

$$a = R_2 R_3 / R_1$$