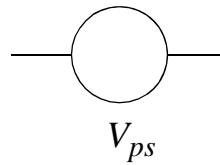


Power Supplies




- DC power supplies can either be direct or generated from AC.
- A generic power source is often indicated by a circle.



- A direct DC source is indicated as a battery (or photocell)



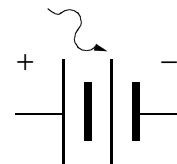
- If the DC source is from a photocell, the symbol will reflect that.



Power Load



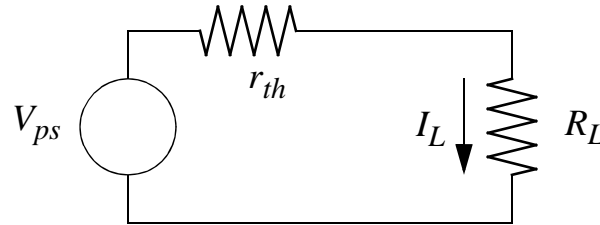- Real power supplies have internal resistance in addition to any resistive load.
- Loads require voltage and draw current from a power supply.
- Power supplies dissipate heat through their internal resistance.



$$P = (I_L)^2 r_{th}$$

- In general power supplies convert voltage from a larger source V_{in} .
- If a supply has a maximum rating of V_{max} , I_{max} , then


$$P = (V_{in} - V_{max}) I_{max}$$

- Many power supplies use metal fins to increase their ability to dissipate heat.

Power Line Interference



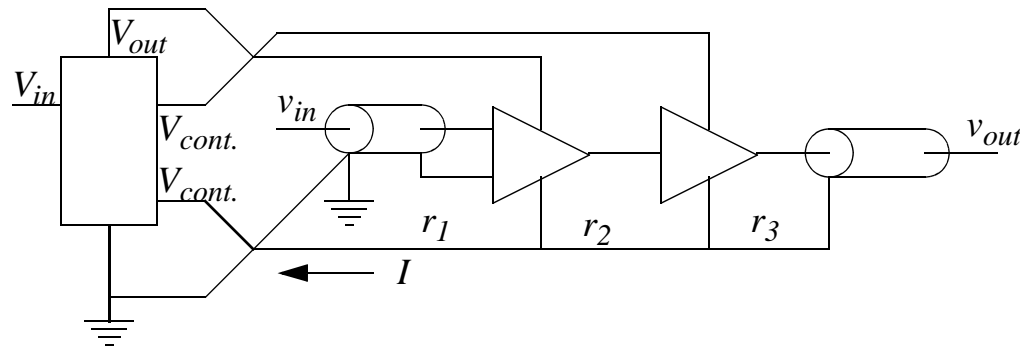
- Loads such as amplifiers draw current.
- Both the power supply and wires have resistance drops.
- Long wires with loops to ground can pick up electromagnetic signals.
- Input signals have frequency-dependent fluctuations.
- Connecting power in series exacerbates the problem.




Improved Power Connections



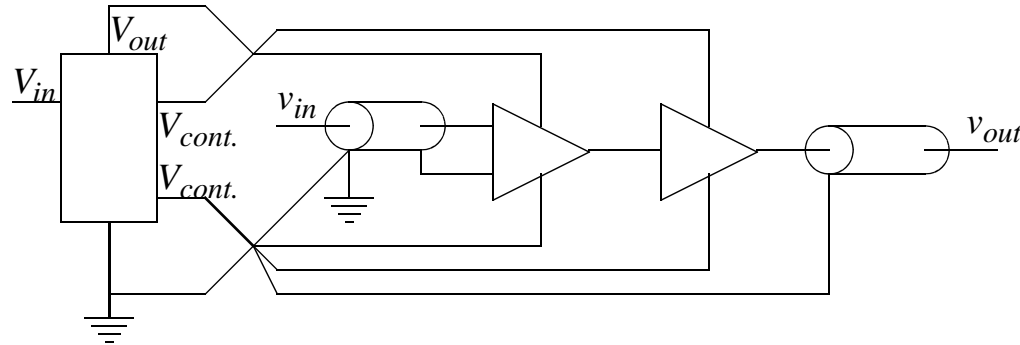- Reconnect common ground and power connections.



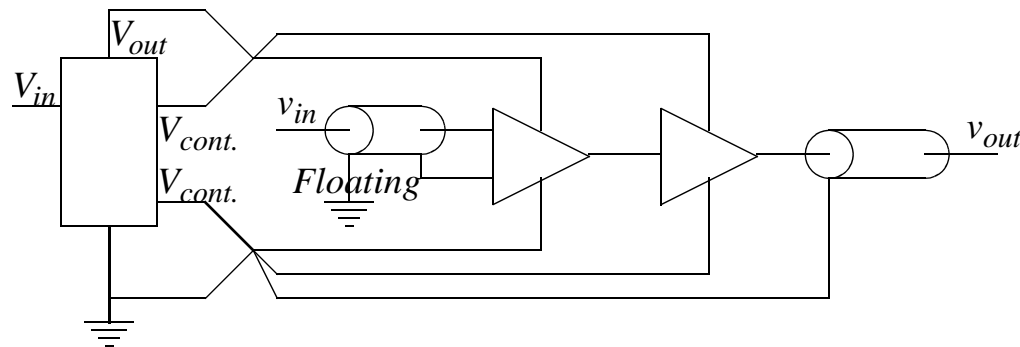
- All power and ground connections are at a single point.
- This prevents voltage drops along wires carrying supply voltage.
- Better can be to float the input ground into amplifiers; keep the difference constant.



AC Conversion




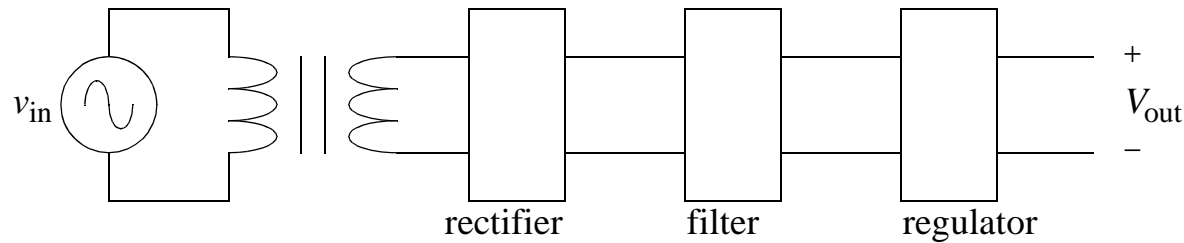- The most common AC to DC supply is a linear AC power supply.



- The input is usually the 120 VAC line voltage.
120 VAC, 60 Hz, 3-conductors: hot neutral and ground.
Always use ground and ground the case of instruments.
- Fuses are used to protect the instruments.
Wall fuses are for fire prevention - too slow to protect electronics.
A slow-blow 1-amp fuse is faster than a 15-amp wall fuse.

Transformers

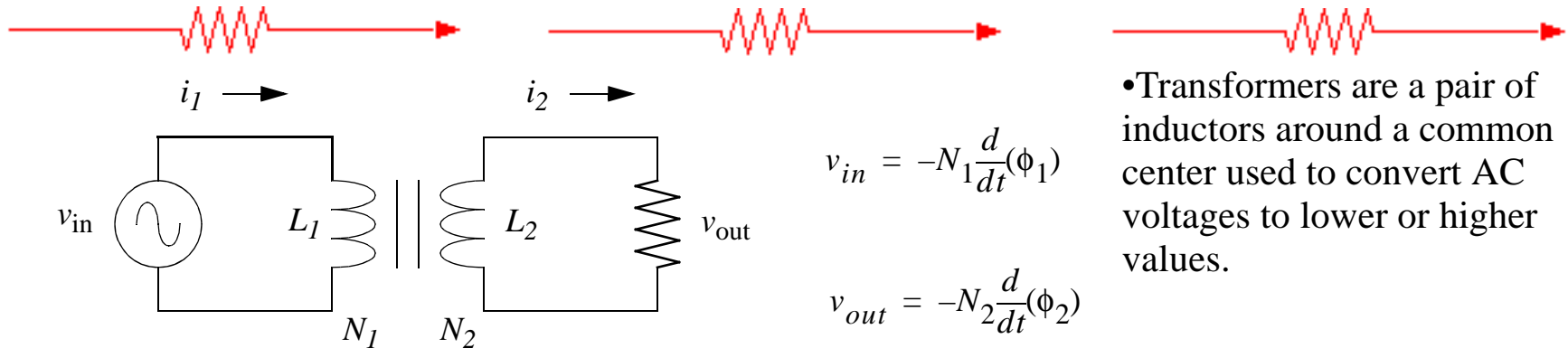

• Transformers are a pair of inductors around a common center used to convert AC voltages to lower or higher values.

- An ideal transformer depends on ratio of turns $n = N_1/N_2$.

$$v_{out}/v_{in} = \frac{N_2}{N_1} = \frac{1}{n} \quad i_{out}/i_{in} = \frac{N_1}{N_2} = n$$

- The input and output impedance changes through a transformer.

$$Z_{in} = \frac{v_{in}}{i_{in}}$$


$$Z_{out} = \frac{v_{out}}{i_{out}}$$

$$Z_{in} = \frac{v_{in}}{i_{in}} = \frac{v_{in}}{i_{in}} \left(\frac{i_{out} v_{out}}{v_{out} i_{out}} \right) = n^2 Z_{out}$$


Rectifier



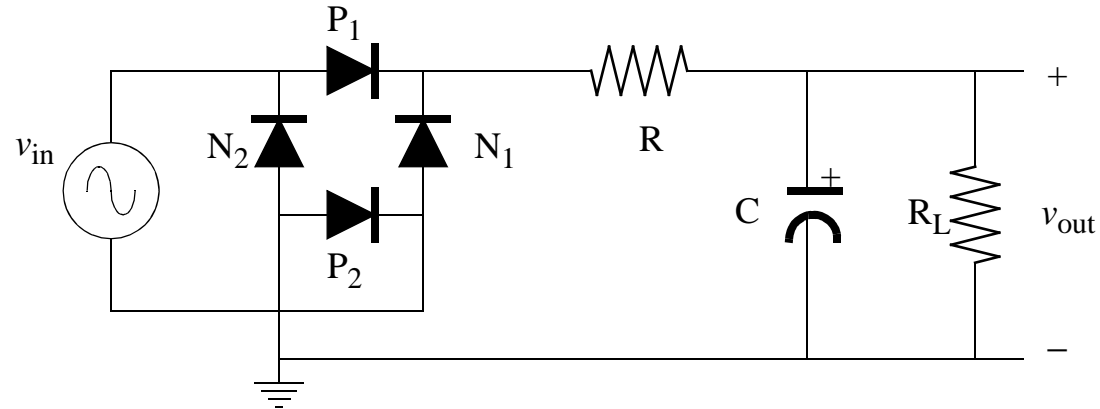- A full wave bridge rectifier is used in an AC to DC converter.
- Combine a full-wave rectifier with a low-pass filter.



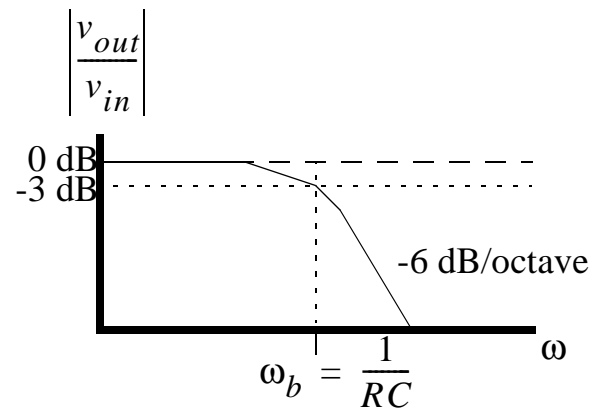
- The low pass filter should have a relatively long time constant $RC \gg \frac{1}{f(v_{in})}$
- The cutoff is illustrated in a low pass Bode plot.



AC Ripple



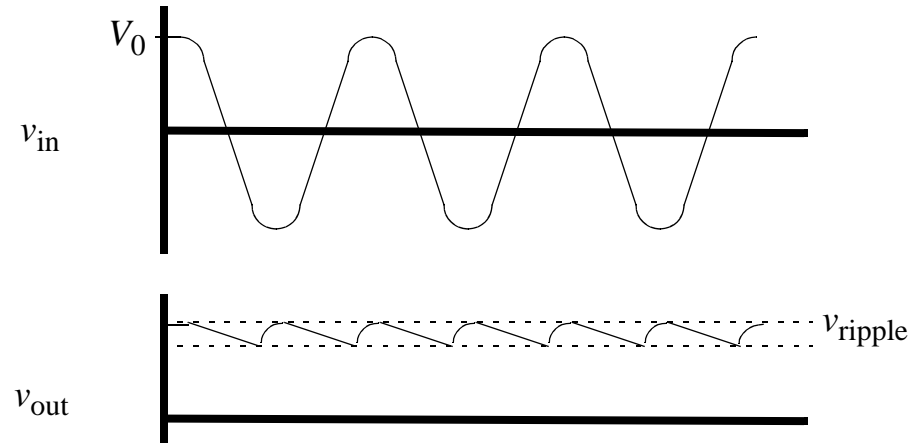- The output will still have a “ripple” proportional to V_0/RCf .




- This is “unregulated” DC.

Switching Power Supply



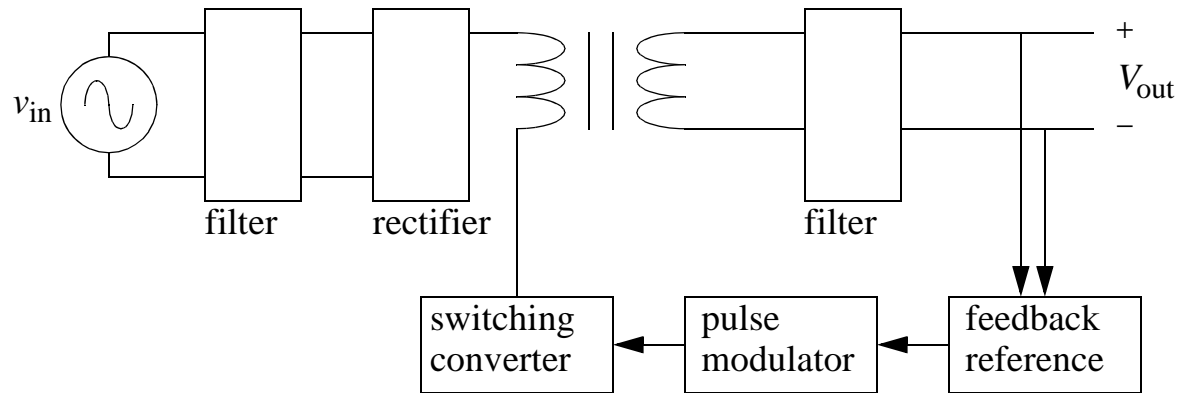
- A switching power supply uses a feedback loop to control the output.



Voltage Regulation



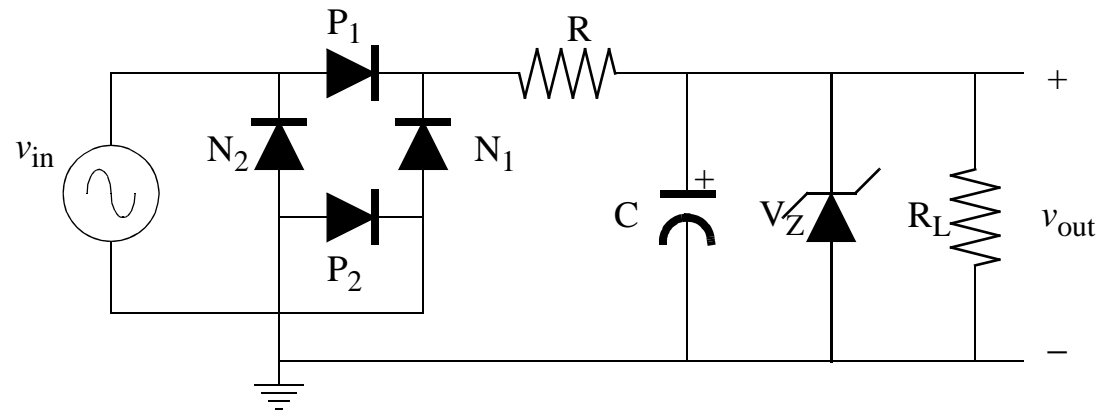
- A zener diode is used to regulate the output voltage
- The zener will draw sufficient current above a minimum to keep the voltage at V_Z .
- A passive voltage regulator uses a zener alone.



- The rectifier must provide enough voltage to allow the zener to regulate, even at the minimum of the ripple.
- The resistor, R , must be small enough to avoid a voltage drop to the zener diode.
- The load will form a voltage divider with the internal resistor R .

Active Voltage Regulator

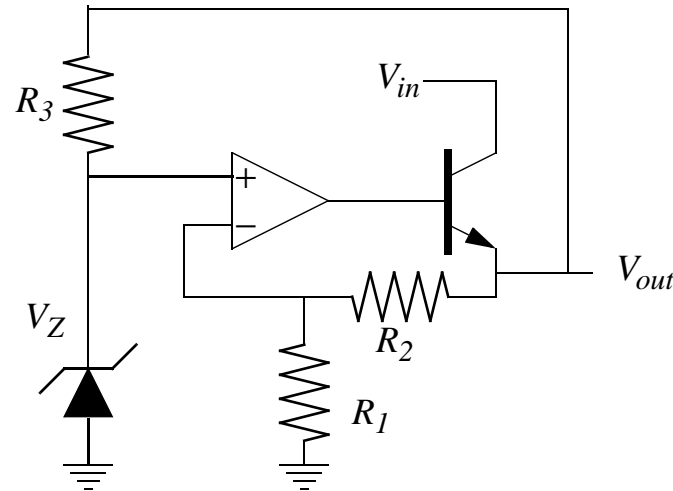- An active voltage regulator uses feedback through an amplifier.




- Negative feedback through R_2 sets the voltage across R_1 equal to V_Z .
- The current through R_1 , also goes through R_2 to set V_{out} .

$$V_{out} = V_Z + \frac{V_Z}{R_1} R_2 = \frac{R_1 + R_2}{R_1} V_Z$$

- R_3 sets the current in the zener diode, no voltage divider with the load.
- This is similar to the 3-terminal regulator, LM7805 by National Semiconductor.

Adjustable Voltage Regulator

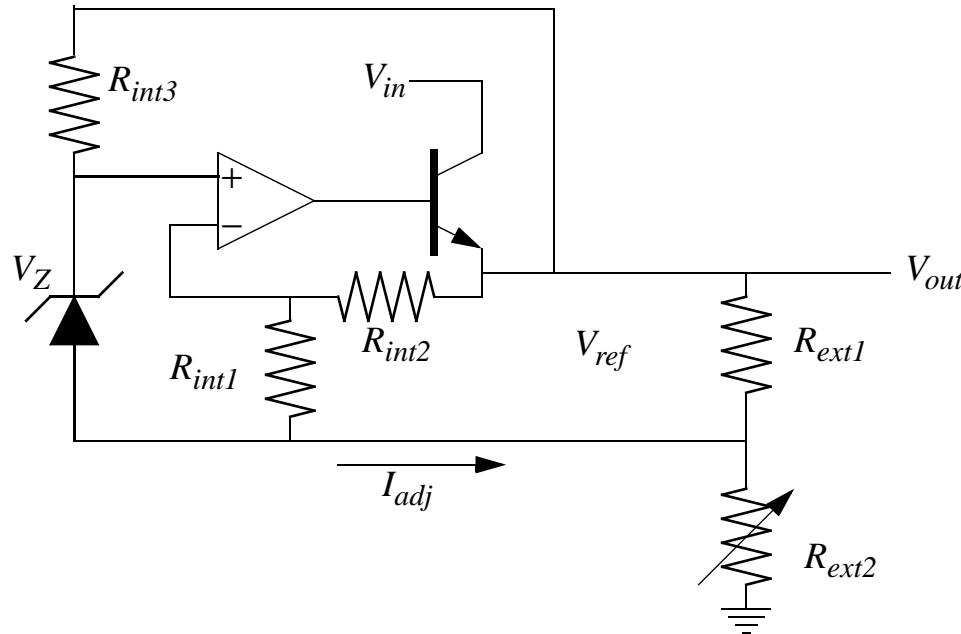- A variable resistor can be used to make an adjustable voltage source.




- The main part of the circuit is a fixed voltage regulator that produces a reference voltage, V_{ref} .
- Current, I_{adj} , through R_{int1} and the zener is a constant based on V_{ref} .
- I_{adj} and V_{ref} set the current flowing through the variable resistor.

$$V_{out} = \frac{R_{ext1} + R_{ext2}}{R_{ext1}} V_{ref} + I_{adj} R_{ext2}$$

- This is essentially the 3-terminal adjustable regulator, LM317.

Short Circuit Protection

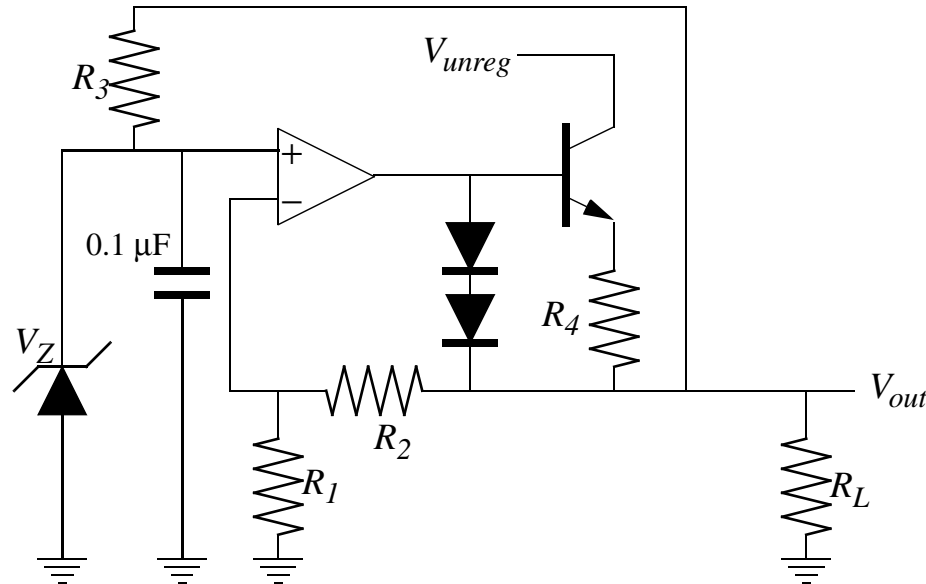- A major need for a power supply is to protect active components from short circuits.
- Diodes are used to prevent shorts damaging the regulator.




$$V_{out} = \frac{R_1 + R_2}{R_1} V_Z$$

- If R_L is near zero, then there would be too much current drawn.
- Diodes allow second path for current from op amp to load.

Current Regulation




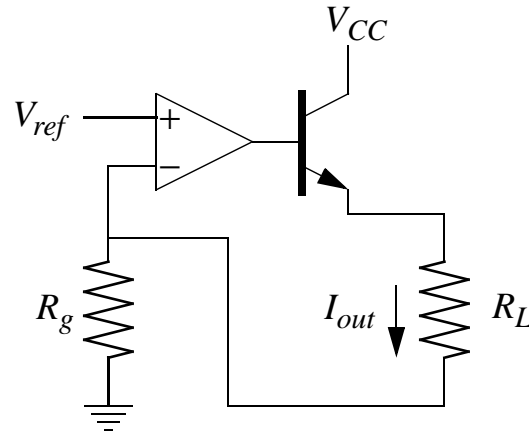- Some circuits require fixed current.
- Transistor current can be controlled by the base voltage.



$$I_{out} = \frac{V_{ref}}{R_g}$$

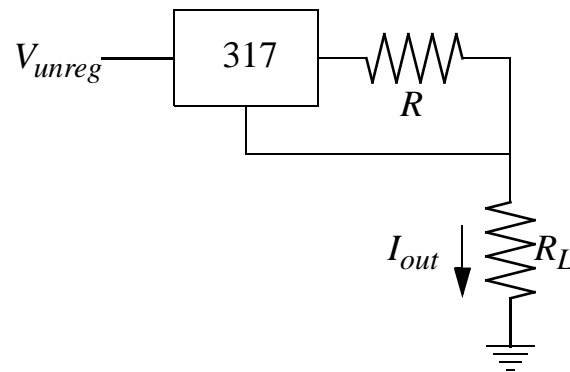- Use a preset voltage regulator through a fixed resistor also sets a current.




$$I_{out} = \frac{1.25V}{R}$$

Voltage Multiplier



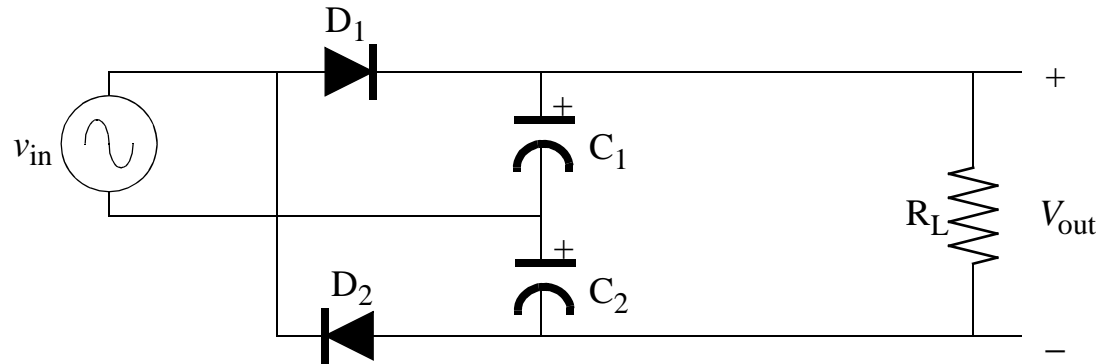- Two half-wave rectifiers in series can double the voltage out.



- When v_{in} is positive the current flows through D_1 , charging C_1 .
- When v_{in} is negative the current flows through D_2 , charging C_2 .
- The available voltage on each capacitor is V_0 so the total $V_{out} = 2V_0$.
- The process can be extended: n capacitors and n diodes gives n times the input peak voltage.
- Power is conserved, so $V_{in}I_{in} = V_{out}I_{out}$.
- For example, 3 A at 120 VAC in could give 3000 V and 120 mA DC out.