Amplifier Circuits



### **Two Rules for Op-amp Circuits**

- **1.**  $I_+ = I_- = 0$ . The input currents are 0.
- 2.  $V_+ V_- = 0$ . The input voltage difference is 0 when there is negative feedback.



#### **Buffer/Follower**

• The simplest buffer is a non-inverting amplifier without resistors.



• Effectively,  $R_1 = \infty$ , and  $R_2 = 0$ . So,  $A = 1 + \frac{R_2}{R_1} = 1$ .

# Switchable Inverter/Follower



- The inverter has a gain of -1.
- The follower shorts the input resistor for a gain of 1 + 0/10k = 1.
- A transistor can be used for the switch:



• The follower setting has  $v_+ = v_{in}$ , since  $Z_{in+}$  is very large;  $v_-$ , and  $v_{out}$  must follow  $v_+$ .

## Follower with Input Filter



• High-pass input filter can be added to a non-inverting amplifier to buffer only high frequencies.



- From the op-amp rule no current flows into  $v_+$ .
- The input current needs a path to ground through  $R_3$ .
- The input impedance is set by the filter  $Re(Z_{in}) = Re(1/j\omega C + R_3) = R_3$ .
- As a complex divider the gain at  $v_+$  is  $A = \frac{1/j\omega C}{1/j\omega C + R_3} = \frac{1}{1+j\omega R_3 C}$ .
- The breakpoint frequency is  $f_B = 1/2\pi R_3 C = 16$  Hz.
- The gain for high frequencies is the same as the remaining follower.

$$A = 1 + \frac{R_2}{R_1} = 1 + \frac{18}{2} = 10$$

## **Bootstrapped Follower**



• The simple buffer/follower has a gain of 1 and large input impedance.



- A high-pass input filter reduces the impedance to be only the impedance of the filter.
- The op-amp follower can add a *bootstrap* capacitor.



• For low frequencies the gain is zero. At high frequencies, the capacitors look like wires. Since  $v_{-} = v_{+}$  from op-amp rule 2, the voltage across the 1 M $\Omega$  resistor is nearly 0, so the current through the resistor is nearly 0. Since input impedance is  $v_{in}/i_{in}$  and  $i_{in}$  is nearly 0, the input impedance is very high.

-~~~

Logarithmic Amplifier





- $R_B$  compensates for the bias current.
- The current  $I_{in}$  is given by  $I_{in} = \frac{V_{in}}{R}$ .
- This current must flow into the collector of the transistor  $I_C = I_0 e^{V_{BE}/V_T} = \frac{V_{in}}{R}$ .
- The base-emitter voltage is equal to the negative of  $V_{out}$ ;  $V_{out} = -V_T \log \frac{V_{in}}{I_0 R}$ .
- The output depends on the logarithm of the input voltage.

#### LABORATORY ELECTRONICS II

**Analog Product** 

- The output of two logarithmic amplifiers can be summed through an inverter.
- An adjustable control voltage compensates for the offsets in the log amplifiers.
- An antilog amplifier reverses the input and feedback stages.
- The result is proportional to the product of the two input voltages.







**\_\_** 



- The output is usually measured in  $V/\mu A$ .
- The op-amp provides low output impedance, hence higher power.

**Current-to-Current Converter** 

\_\_\_\_\_





-^^^

$$V_{out} = -R_f I_{in}$$

From Kirchoff's Laws:

$$I_g = I_L + I_{in}$$
$$V_{out} = R_g I_g$$

Combine the equations:

$$I_L = -I_{in} \left( 1 + \frac{R_f}{R_g} \right)$$

Voltage-to-Current Converter



• An op-amp follower can be used to drive a conventional transistor current source.



- The current  $I_{out}$  splits through the FET and BJT.
- No current passes through the gate of the FET or the  $v_1$  op-amp input.
- All current  $I_{out}$  is present through the resistor  $I_R$ .
- $V_E = V_{in}$  from the op-amp voltage rule.

$$I_{out} = -\frac{V_{in}}{R}$$



• An amplifier can utilize the relation between charge and current.

$$I = \frac{dQ}{dt} = C\frac{dV}{dt}$$



• The current is converted to a voltage.

$$v_{out} = -iR_f = -R_f C_i \frac{dv_{in}}{dt}$$

• For a sinusoidal input  $v_{in} = V_0 \sin \omega t$ ,

$$\frac{dv_{in}}{dt} = V_0 \omega \cos \omega t$$

$$v_{out} = -R_f C_i V_0 \omega \cos \omega t = -R_f C_i \omega v_{in}$$

• The amplitude increases with increasing frequency.







• Solving for *v<sub>out</sub>*:

$$v_{out} = \frac{-1}{R_i C_f} \int v_{in} dt + K$$

• With a sine wave input

$$v_{out} = \frac{-1}{\omega R_i C_f} v_{in} + K$$

• The amplitude decreases with frequency.

# Stabilized Integrator

• The constant term from the integral is undesirable on the output.

\_\_\_\_\_MM^

- A switch can be used to discharge the capacitor.
- The circuit can provide a path for the capacitor to discharge.



• The feedback resistor and capacitor have a parallel impedance

$$Z_f = \frac{R_f}{1 + j\omega R_f C_f}$$

- The breakpoint frequency is  $f = 1/2\pi RC = 0.007$  Hz.
- Only DC can feedback for amplification.

# Limited Differentiator

• Differentiator has large amplification at high frequencies.

- A high frequency cutoff above the signal range is often needed.
- Combine an integrator and differentiator.



• The differentiator has a low cutoff

$$v_{out} = -R_f C_i \frac{dv_{in}}{dt}$$
  $f_B = \frac{1}{2\pi R_f C_i} = 160 Hz$ 

• The integrator begins working at

$$v_{out} = \frac{-1}{R_i C_f} \int v_{in} dt$$
  $f_B = \frac{1}{2\pi R_i C_f} = 3MHz$ 

• The differentiator will perform well between those two frequencies.

-////